

Name: Xinyu Hadrian Hu, and Duan Wei Zhang

Student Number: 500194233, and 500824903

TA: Jasminder Singh

Date: June 28, 2020

COE 608: Computer Architecture and Design

---

## **COE 608: Lab 4, Part 2 Report**

### **Objective**

The purpose of this lab is to put together everything we have done so far, with the addition of the upper zero extender, lower zero extender, and reducer with the program counter, arithmetic logical unit, multiplexers, and operational inverters into a functioning data-path for the MIPS instructional set architecture.

### **Design and Implementation**

I first started with the reducers, LZE and UZE implementations. I did the data-path last. The following truth-tables provide examples of some of the purposes of the LZE, UZE, and reducer. The LZE extends zeroes by padding the bits from 15 down to 0. The UZE does the inverse of the LZE operation by padding zeroes from 31 down to 16. The reducer helps to reduce a 32-bit data into 8-bit data. The data-path is programmed in VHDL using the structural behavior, by utilizing port mapping and signals to denote the wires and buses between the many devices used throughout the course.

The truth tables for each of the new devices are illustrated in the following pages.

See the following figures below: Figure 1: UZE Truth Table, Figure 2: LZE Truth Table, Figure 3: Reducer Truth Table and Figure 4: Data-path signals truth table.

Upper Zero Extender	
In (hex)	Out (hex)
0 0 0 0 0 0 0 1	0 0 0 0 0 0 0 0
0 0 0 0 0 0 0 A	0 0 0 0 0 0 0 0
0 0 0 F 9 E D F	0 0 0 F 0 0 0 0
A B C 8 5 F G 1	A B C 8 0 0 0 0

Figure 1: UZE Truth Table

Next, is the Lower Zero Extender Truth Table:

Lower Zero Extender	
In (hex)	Out (hex)
0 0 0 0 0 0 0 1	0 0 0 0 0 0 0 0 1
0 0 0 0 0 0 0 A	0 0 0 0 0 0 0 0 A
0 0 0 F 9 E D F	0 0 0 0 0 9 E D F
A B C 8 5 F G 1	0 0 0 0 0 5 F G 1

Figure 2: LZE Truth Table

Next, is the Reducer Truth Table:

Reducer	
In (hex)	Out (hex)
0 0 0 0 0 0 0 1	0 1
0 0 0 0 0 0 0 A	0A
0 0 0 F 9 E D F	9 E D F
A B C 8 5 F G 1	5 F G 1

Figure 3: Reducer Truth Table

Finally, the Data-path Truth Table:

Name: Xinyu Hadrian Hu		Student #: 500194233		Section: 01								
INST	CLR_IR LD_IR	LD_PC INC_PC	CLR_A LD_A	CLR_B LD_B	CLR_C LD_C	CLR_Z LD_Z	ALU OP	EN WEN	A/B MUX	REG MUX	Data MUX	IM_MUX1 IM_MUX2
LDA	00	00	01	00	00	00	XXX	10	0/X	X	1	X
LDB	00	00	00	01	00	00	XXX	10	X/0	X	1	X
STA	00	00	00	00	00	00	XXX	11	X	0	X	X
JMP	00	00	00	00	00	00	XXX	11	X	1	X	X
STAB	00	10	00	00	00	00	XXX	X	X	X	X	X
LDAL	00	00	01	00	00	00	XXX	X	1/X	X	X	X
LDBI	00	00	00	01	00	00	XXX	X	X/1	X	X	X
LUI	00	00	01	10	00	00	1	X	0/X	X	10	1/X
ANDI	00	00	01	00	01	01	0	X	0/X	X	10	0/01
DECA	00	00	01	00	01	01	110	X	0/X	X	10	0/10
AND	00	00	01	00	01	01	10	X	0/X	X	10	0/00
ADDI	00	00	01	00	01	01	110	X	0/X	X	10	0/00
SUB	00	00	01	00	01	01	10	X	0/X	X	10	0/10
INCA	00	00	01	00	01	01	0	X	0/X	X	10	0/00
ORI	00	00	01	00	01	01	10	X	0/X	X	10	0/01
ROL	00	00	01	00	01	01	1	X	0/X	X	10	0/01
ROR	00	00	01	00	01	01	100	X	0/X	X	10	0/X
CLRA	00	00	01	00	01	01	101	X	0/X	X	10	0/X
CLRC	00	00	10	00	00	00	XXX	X	X	X	X	X
CLRZ	00	00	00	10	00	00	XXX	X	X	X	X	X
PC <= PC + 4	00	10	00	00	00	00	XXX	X	X	X	X	X
IR <= M[INT]	01	00	00	00	00	00	XXX	X	X	X	0	X
PC IR [15..0]	00	10	00	00	00	00	XXX	X	X	X	X	X

Figure 4: Data-path signals truth table

## Observations and Results

Below are the functional and timing waveforms derived for each of the new components listed for this lab.

The following figures are the observations of this project:

Figure 5: LZE Functional Waveform, Figure 6: LZE Timing Waveform, Figure 7: UZE Functional Waveform, Figure 8: UZE Timing Waveform, Figure 9: Reducer Functional Waveform, Figure 10: Reducer Timing Waveform, Figure 11: Data-path Random Input Waveform, Figure 12: Data-path Output Functional Waveform, and Figure 13: Data-path Output Timing Waveform are the figures of interest.

LZE: Functional and Timing

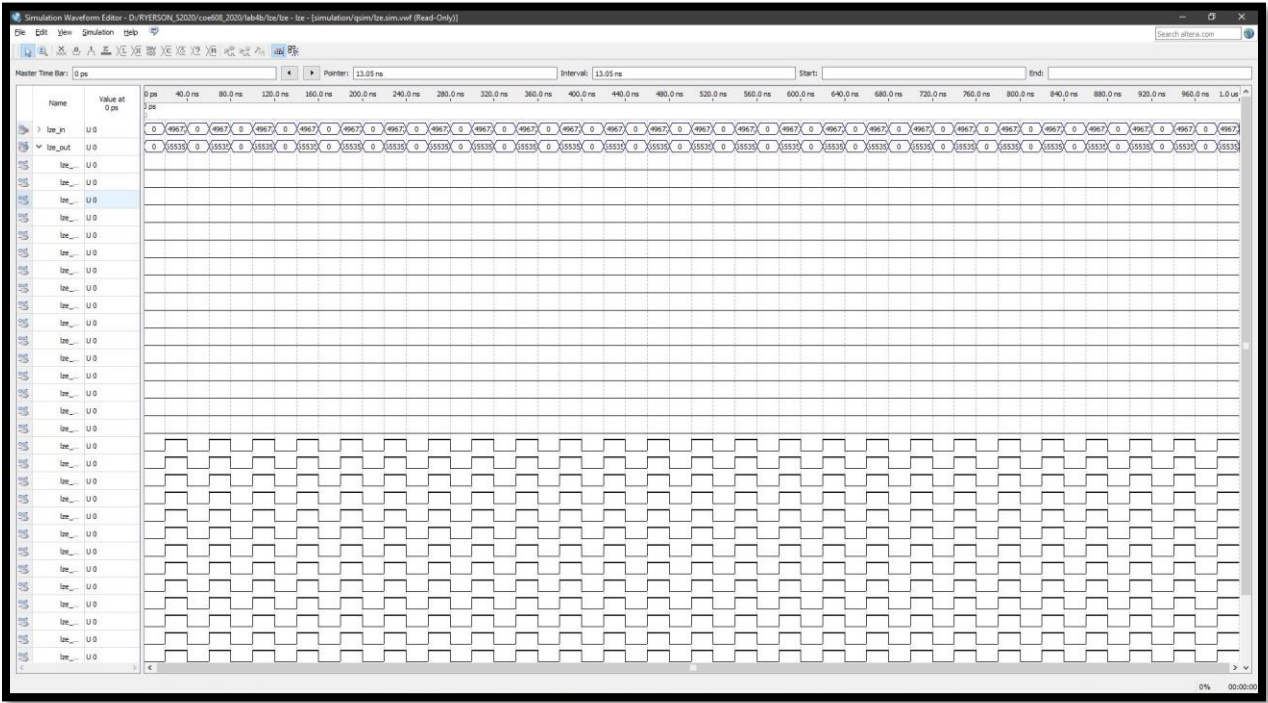


Figure 5: LZE Functional Waveform

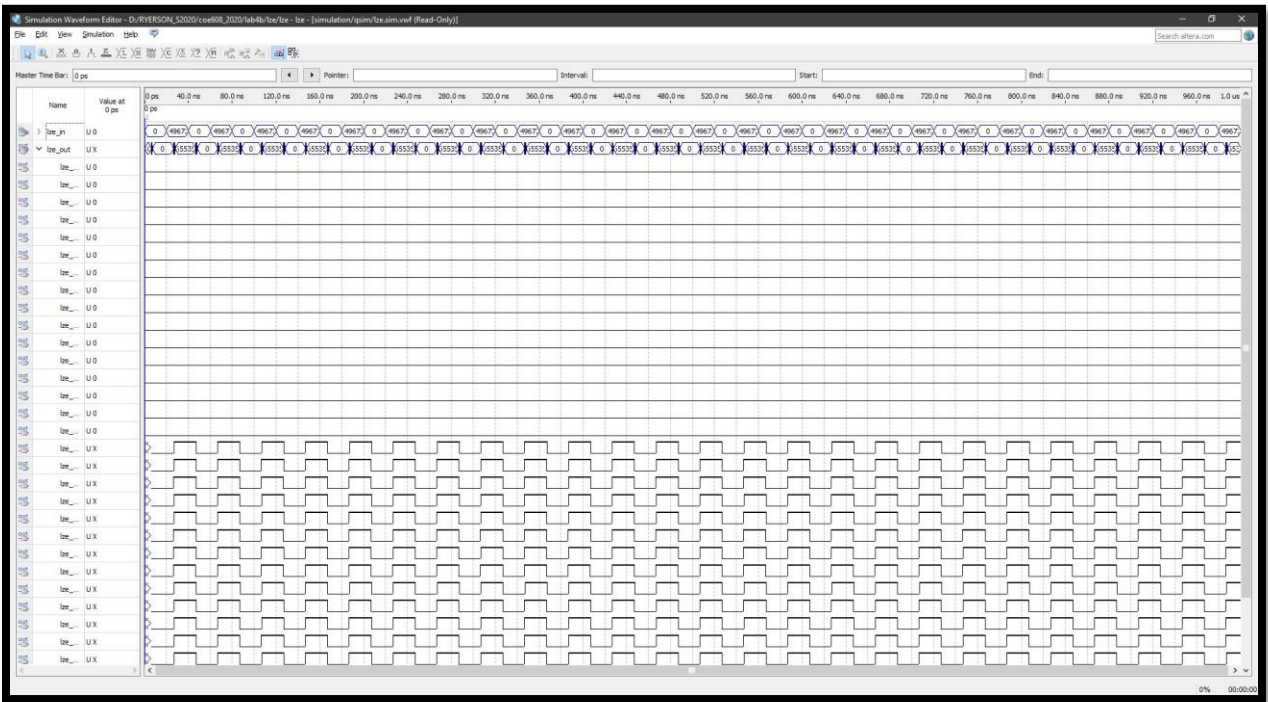


Figure 6: LZE Timing Waveform

**UZE: Functional and Timing**

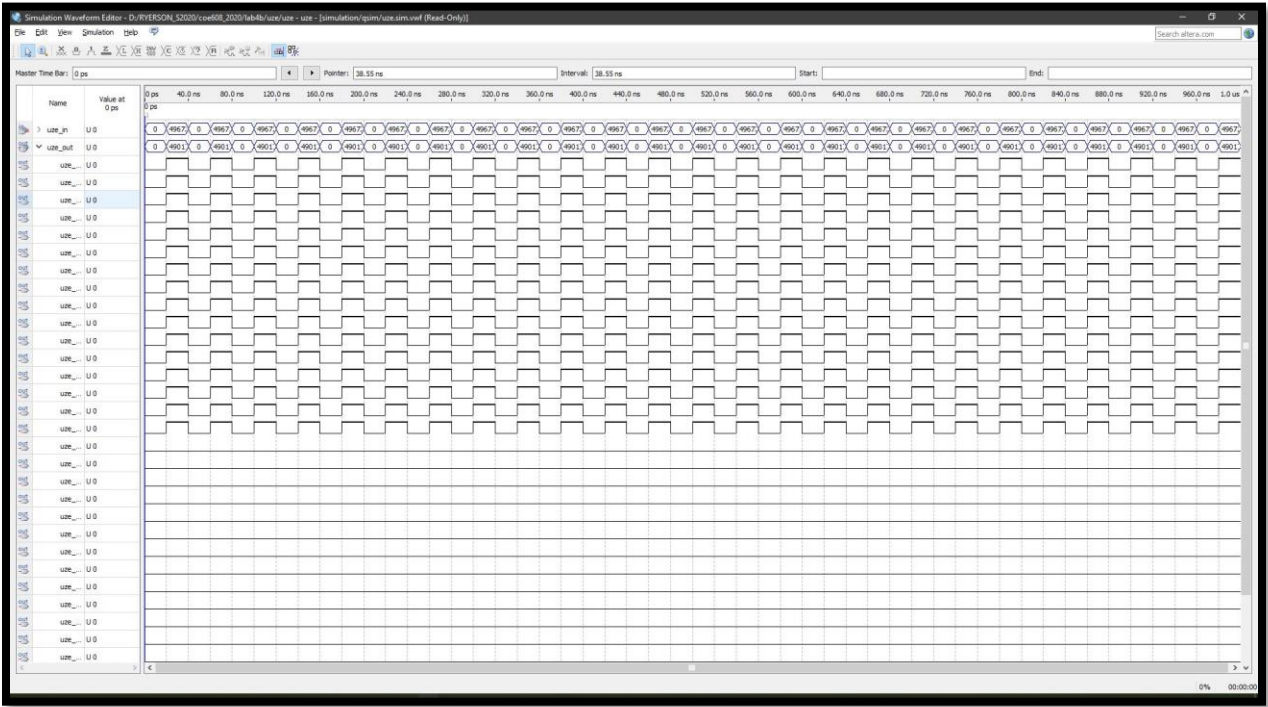


Figure 7: UZE Functional Waveform

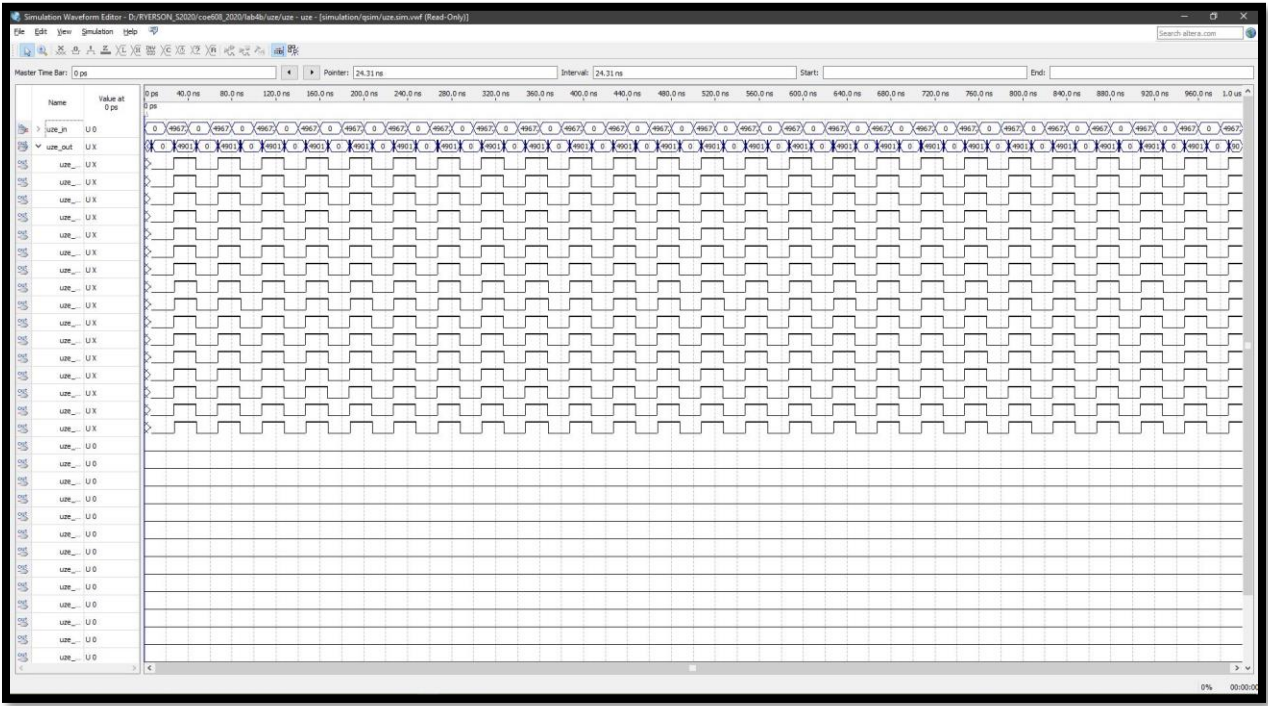


Figure 8: UZE Timing Waveform



## Reducer: Functional and Timing



Figure 9: Reducer Functional Waveform



Figure 10: Reducer Timing Waveform

## Data-path: Functional and Timing



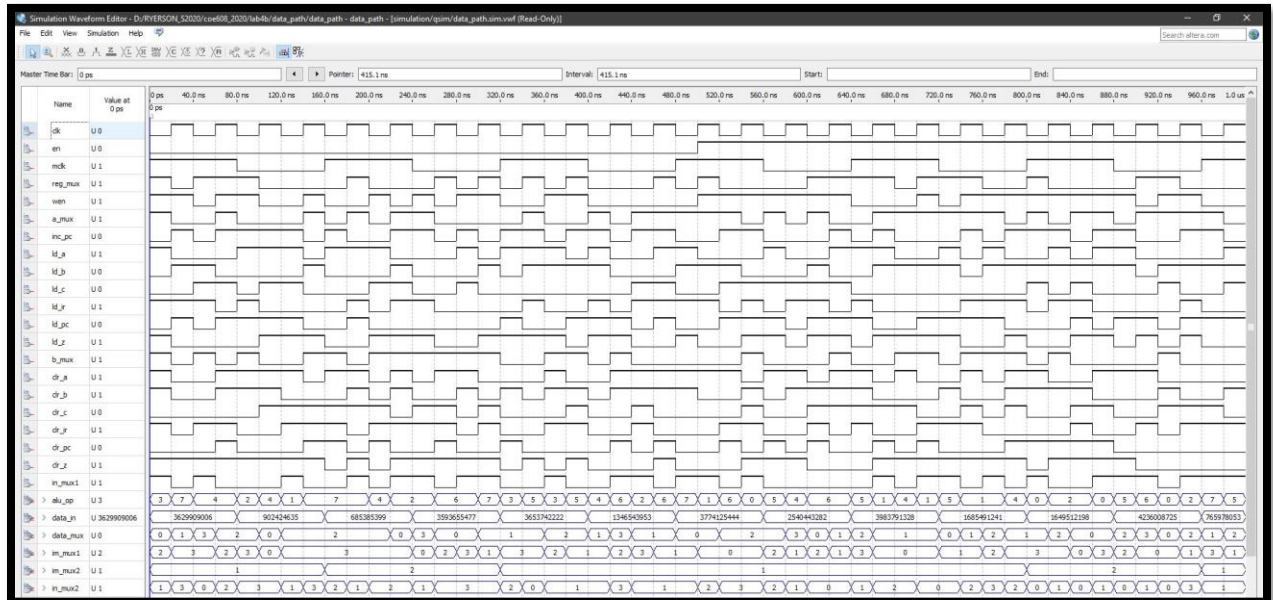


Figure 11: Data-path Random Input Waveform

 

*Figure 12: Data-path Output Functional Waveform*

 

*Figure 13: Data-path Output Timing Waveform*

## **Discussions and Conclusions**

The data-path implements INCA, ADDI, LDBI and LDA operations by using a finite state machine to select these advanced operations.

The main determinant of the data-path speed is the longest operation performed. In this case, the worst-case timing depends on the operation that is most time-consuming. From Figure 13, it appears the worst-case delay is 10 ns.

The most reliable limit for the data-path clock is 10 ns.

## **Appendix: VHDL Codes and Screenshots of Waveforms**

I have provided the VHDL and screenshots of the waveforms for easier reading.

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  use ieee.std_logic_unsigned.all;
5
6  entity data_path is
7      port(
8          --clock and memory clock
9          clk, mclk : in std_logic;
10         --memory signals
11         wen, en: in std_logic;
12         --register control signals
13         clr_a, ld_a: in std_logic;
14         clr_b, ld_b: in std_logic;
15         clr_c, ld_c: in std_logic;
16         clr_z, ld_z: in std_logic;
17         clr_pc, ld_pc: in std_logic;
18         clr_ir, ld_ir: in std_logic;
19         --register outputs
20         out_a, out_b: out std_logic_vector(31 downto 0);
21         out_c, out_z: out std_logic;
22         outp, out_ir: out std_logic_vector(31 downto 0);
23         --pc special input
24         inc_pc: in std_logic;
25         --address and data bus signal debug
26         addr_out : inout std_logic_vector(31 downto 0);
27         data_in: in std_logic_vector(31 downto 0);
28         DATA_BUS, mem_out, mem_in: inout std_logic_vector(31 downto 0);
29         in_mux1: in std_logic;
30         in_mux2: in std_logic_vector(1 downto 0);
31         --alu op
32         alu_op: in std_logic_vector(2 downto 0);
33         --mux controllers
34         data_mux : in std_logic_vector(1 downto 0);
35         reg_mux: in std_logic;
36         a_mux, b_mux: in std_logic;
37         im_mux1, im_mux2: in std_logic_vector(1 downto 0));
38 end data_path;
39
40 architecture description of data_path is
41     --components
42
43     component alu
44     port(
45         a, b: in std_logic_vector(31 downto 0);
46         op: in std_logic_vector(2 downto 0);
47         result: inout std_logic_vector(31 downto 0);
48         cout: out std_logic;
49         zero: out std_logic);
50 end component alu;
51
52     component register1
53     port(
54         d,ld,clr,clk: in std_logic;
55         Q: out std_logic);
56 end component register1;
57
58     component register32
59     port(
60         d: in std_logic_vector(31 downto 0);
61         ld,clr,clk: in std_logic;
62         Q: out std_logic_vector(31 downto 0));
```




```


63     end component register32;
64
65     component pc
66     port(
67         clr, clk, ld, inc: in std_logic;
68         d: in std_logic_vector(31 downto 0);
69         q: inout std_logic_vector(31 downto 0));
70     end component pc;
71
72     component memoryModule
73     port (
74         clk: in std_logic;
75         addr: in unsigned(7 downto 0);
76         data_in : in std_logic_vector(31 downto 0);
77         wen, en: in std_logic;
78         data_out: out std_logic_vector(31 downto 0));
79     end component memoryModule;
80
81     component lze
82     port(
83         lze_in: in std_logic_vector(31 downto 0);
84         lze_out: out std_logic_vector(31 downto 0));
85     end component lze;
86
87     component uze
88     port(
89         uze_in : in std_logic_vector(31 downto 0);
90         uze_out: out std_logic_vector(31 downto 0));
91     end component uze;
92
93     component red
94     port(
95         red_in : in std_logic_vector(31 downto 0);
96         red_out : out unsigned(7 downto 0));
97     end component red;
98
99     component mux2to1
100    port (
101        s : in std_logic;
102        w0, w1 : in std_logic_vector(31 downto 0);
103        f: out std_logic_vector(31 downto 0));
104    end component mux2to1;
105
106    component mux4to1
107    port (
108        s : in std_logic_vector(1 downto 0);
109        x0, x1, x2, x3 : in std_logic_vector(31 downto 0);
110        f : out std_logic_vector(31 downto 0));
111    end component mux4to1;
112
113    --signals
114
115    signal IR_out, data_bus1, lze_pc_out, lze_Amux_out, lze_Bmux_out, Amux_out, Bmux_out,
    registerA_out, registerB_out, registerMux_out, memory_out : std_logic_vector(31 downto 0);
116    signal uze_imMUX1_out, imMUX1_out, lze_imMUX2_out, imMUX2_out, alu_out : std_logic_vector
    (31 downto 0);
117    signal red_DataMem_out: unsigned(7 downto 0);
118    signal zero_flag, carry_flag : std_logic;
119    signal temp : std_logic_vector(30 downto 0) := (others => '0');
120    begin
121        ir_register : register32 port map (data_bus, ld_ir, clr_ir, clk, IR_out);
122        a_register: register32 port map (Amux_out, ld_a, clr_a, clk, registerA_out);

```

```
123         b_register: register32 port map(Bmux_out, ld_b, clr_b, clk, registerB_out);
124         alu_component: alu port map(imMux1_out, imMUX2_out, alu_op, alu_out, carry_flag,
zero_flag);
125         memory_component: memoryModule port map (mclk, RED_DataMem_out, registerMux_out,
wen, en, memory_out);
126         DATA_BUS <= data_bus1;
127         lze_pc : lze port map (IR_out, lze_pc_out);
128         lze_A_mux : lze port map (IR_out, lze_Amux_out);
129         A_mux0 : mux2to1 port map (a_mux, data_bus, lze_Amux_out, Amux_out);
130         lze_B_mux : lze port map (IR_out, lze_Bmux_out);
131         B_mux0: mux2to1 port map (b_mux, data_bus, lze_Bmux_out, Bmux_out);
132         reg_mux0: mux2to1 port map (reg_mux, registerA_out, registerB_out, registerMux_out
);
133         RED_DATA_MEM: red port map (IR_out, red_DataMem_out);
134         UZE_IM_MUX1: uze port map (IR_out, UZE_imMUX1_out);
135         IM_MUX1a : mux2to1 port map (in_mux1, registerA_out, UZE_imMUX1_out, imMUX1_out);

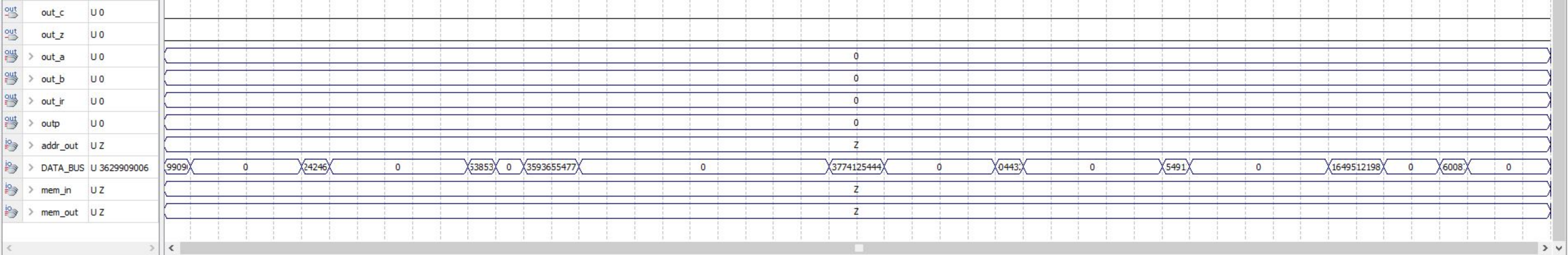136         LZE_IM_MUX2 : lze port map (IR_out, LZE_imMUX2_out);
137         IM_MUX2a : mux4to1 port map (in_mux2, registerB_out, LZE_imMUX2_out, (temp & '1'),
(others => '0'), imMUX2_out);
138         DATA_MUX0: mux4to1 port map (data_mux, data_in, memory_out, alu_out, (others => '0'
), data_bus1);
139         end description;
140
141
142
143
144
145
146
```



 

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4
5  entity lze is
6      port(
7          lze_in: in std_logic_vector(31 downto 0);
8          lze_out: out std_logic_vector(31 downto 0));
9  end lze;
10
11 architecture behavior of lze is
12     signal zeros : std_logic_vector(31 downto 16) := (others => '0');
13     begin
14         lze_out <= zeros & lze_in(15 downto 0);
15     end behavior;
16
17
```



End:

0% 00:00:00







Point

0 ps	40.0 ns	80.0 ns	120.0 ns	160.0 ns	200.0 ns	240.0 ns	280.0 ns	320.0 ns	360.0 ns	400.0 ns	440.0 ns	480.0 ns	520.0 ns	560.0 ns	600.0 ns	640.0 ns	680.0 ns	720.0 ns	760.0 ns	800.0 ns	840.0 ns	880.0 ns	920.0 ns	960.0 ns	1.0 us																								
0 ps																																																	
0	1	2	3	0	1	2	3	0	1	2	3	0	1	2	3	0	1	2	3	0	1	2	3	0	1	2	3	0	1	2	3	0	1	2	3	0	1												
0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25	26	27	28	29	30	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45	46	47	48	49
0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24																									
0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24																									
0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24																									
0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24																									



0 ns	
2	
6	
	3
	1


```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4
5  entity mux4to1 is
6      port
7          (s : in std_logic_vector(1 downto 0);
8           x0, x1, x2, x3 : in std_logic_vector(31 downto 0);
9           f : out std_logic_vector(31 downto 0));
10 end mux4to1;
11
12 architecture behavior of mux4to1 is
13     begin
14         with s select
15             f <= x0 when "00",
16                 x1 when "01",
17                 x2 when "10",
18                 x3 when "11";
19 end behavior;
20
21
22
```



```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity red is
6      port(
7          red_in : in std_logic_vector(31 downto 0);
8          red_out : out unsigned(7 downto 0));
9  end red;
10
11 architecture behavior of red is
12     begin
13         red_out <= unsigned(red_in(7 downto 0));
14     end behavior;
15
16
```




 Master Time Bar: 0 ps Pointer: 1.19 ns Interval: 1.19 ns Start: End:





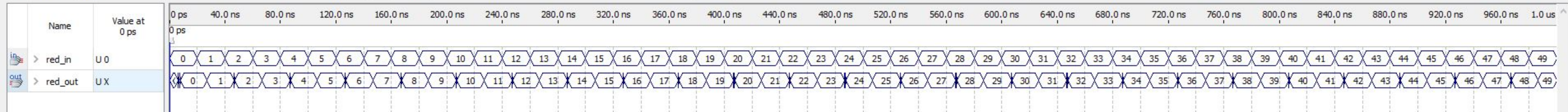Master Time Bar: 0 ps    Pointer:    Interval:    Start:    End:



```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4
5  entity uze is
6      port(
7          uze_in : in std_logic_vector(31 downto 0);
8          uze_out: out std_logic_vector(31 downto 0));
9  end uze;
10
11 architecture behavior of uze is
12     signal zeros : std_logic_vector(15 downto 0) := (others => '0');
13     begin
14         uze_out <= uze_in(31 downto 16) & zeros;
15     end behavior;
16
17
```

Master Time Bar: 0 ps    Pointer: 38.55 ns    Interval: 38.55 ns    Start:    End:

The figure is a timing diagram with a time axis from 0 ps to 1.0 us. The left panel lists 24 signals: uze\_in, uze\_out, and 22 signals named uze\_... (uze\_0 to uze\_21). The right panel shows the waveforms for these signals. The top two signals, uze\_in and uze\_out, have data values displayed in hexagonal boxes above their waveforms. The uze\_in signal has values alternating between 0 and 4967. The uze\_out signal has values alternating between 0 and 4901. The remaining 22 uze\_... signals show square wave patterns with varying duty cycles and phases. The uze\_0 signal has a 50% duty cycle. The uze\_1 signal has a 25% duty cycle. The uze\_2 signal has a 75% duty cycle. The uze\_3 signal has a 50% duty cycle. The uze\_4 signal has a 25% duty cycle. The uze\_5 signal has a 75% duty cycle. The uze\_6 signal has a 50% duty cycle. The uze\_7 signal has a 25% duty cycle. The uze\_8 signal has a 75% duty cycle. The uze\_9 signal has a 50% duty cycle. The uze\_10 signal has a 25% duty cycle. The uze\_11 signal has a 75% duty cycle. The uze\_12 signal has a 50% duty cycle. The uze\_13 signal has a 25% duty cycle. The uze\_14 signal has a 75% duty cycle. The uze\_15 signal has a 50% duty cycle. The uze\_16 signal has a 25% duty cycle. The uze\_17 signal has a 75% duty cycle. The uze\_18 signal has a 50% duty cycle. The uze\_19 signal has a 25% duty cycle. The uze\_20 signal has a 75% duty cycle. The uze\_21 signal has a 50% duty cycle.

Signal	Value at 0 ps
uze_in	U 0
uze_out	U 0
uze_0	U 0
uze_1	U 0
uze_2	U 0
uze_3	U 0
uze_4	U 0
uze_5	U 0
uze_6	U 0
uze_7	U 0
uze_8	U 0
uze_9	U 0
uze_10	U 0
uze_11	U 0
uze_12	U 0
uze_13	U 0
uze_14	U 0
uze_15	U 0
uze_16	U 0
uze_17	U 0
uze_18	U 0
uze_19	U 0
uze_20	U 0
uze_21	U 0



Master Time Bar: 0 ps    Pointer: 24.31 ns    Interval: 24.31 ns    Start:    End:

