

Name: Xinyu Hadrian Hu, and Duan Wei Zhang

Student Number: 500194233, and 500824903

Date: June 26, 2020

COE 608: Computer Architecture and Design

COE 608: Lab 3, Part 2 Report

Purpose

The purpose of this lab is to generate the components of an 8-bit ALU, with six different operations. The addition and subtraction units must be done in structural form of VHDL. We also have to include the seven-segment display driver into the build for this ALU. This is a simplified version of the 32-bit ALU for testing before implementing the 32-bit ALU.

Design and Implementation

The following: Figure 1, Figure 2, Figure 3, and Figure 4 are the 8-bit ALU, operational inverter, BCD to seven-segment display driver, and the 8-bit register codes needed for the function of the 8-bit ALU. The truth table for the 8-bit ALU is from the waveforms generated in Quartus II. The values of the 8-bit register are placed as HEX values for the input and output of d and Q, respectively, otherwise the table will be unreasonably large and unhelpful to the reader. There is no need to show the 8-bit adder, since the operations of the 8-bit adder is the same as those of the 32-bit and 1-bit adders from the previous lab 3a.

8-bit ALU			
OP Name ▼	Neg/Tsel ▼	ALU-Select ▼	Operation Performed ▼
AND (logical)	0	0 0	Result \leq a AND b
OR (logical)	0	0 1	Result \leq a OR b
ADD	0	1 0	Result \leq a + b
SUB	1	1 0	Result \leq a - b
ROL	1	0 0	Result \leq a << 1
ROR	1	0 1	Result \leq a >> 1

Figure 1: 8-bit ALU Truth Table

Op Inverter	
OP	not OP
0	1
1	0

Figure 2: Op Inverter Truth Table

BCD to 7 segment display		
BCD Code	7seg Code	Symbol
0 0 0 0	0 0 0 0 0 0 1	0
0 0 0 1	1 0 0 1 1 1 1	1
0 0 1 0	0 0 1 0 0 1 0	2
0 0 1 1	0 0 0 0 1 1 0	3
0 1 0 0	1 0 0 1 1 0 0	4
0 1 0 1	0 1 0 0 1 0 0	5
0 1 1 0	0 1 0 0 0 0 0	6
0 1 1 1	0 0 0 1 1 1 1	7
1 0 0 0	0 0 0 0 0 0 0	8
1 0 0 1	0 0 0 0 1 0 0	9
1 0 1 0	0 0 0 1 0 0 0	A
1 0 1 1	1 1 0 0 0 0 0	B
1 1 0 0	0 1 1 0 0 0 1	C
1 1 0 1	1 0 0 0 0 1 0	D
1 1 1 0	0 1 1 0 0 0 0	E
1 1 1 1	0 1 1 1 0 0 0	F

Figure 3: BCD to 7-segment display converter Truth Table

8 bit register									
clk		clr		ld		d (hex)		Q (hex)	
0		0		1		0 0		0 0	
1		0		1		0 1		0 1	
0		0		1		0 2		0 1	
1		0		1		0 3		0 3	
0		0		1		0 4		0 3	
1		0		1		0 5		0 5	
0		0		1		0 6		0 5	
1		0		1		0 7		0 7	
0		0		1		0 8		0 7	
1		0		1		0 9		0 9	
0		0		1		0 A		0 9	
1		0		1		0 B		0 B	
0		0		1		0 C		0 B	
1		0		1		0 D		0 D	
0		0		1		0 E		0 D	
1		0		1		0 F		0 F	
0		0		1		1 0		0 F	
1		0		1		1 1		1 1	
0		0		1		1 2		1 1	
1		0		1		1 3		1 3	
0		0		1		1 4		1 3	
1		0		1		1 5		1 5	
0		0		1		1 6		1 5	
1		0		1		1 7		1 7	
0		0		1		1 8		1 7	
1		1		1		1 9		0	
0		1		1		2 A		0	
1		1		1		2 B		0	
0		1		1		2 C		0	
1		1		1		2 D		0	
0		1		1		2 E		0	
1		1		1		2 F		0	
0		1		1		3 0		0	
1		1		1		3 1		0	

Figure 4: 8-bit register Truth Table

The final implementation of the 8-bit ALU in block diagram, schematic format is shown in the next page:

See Figure 5 below.

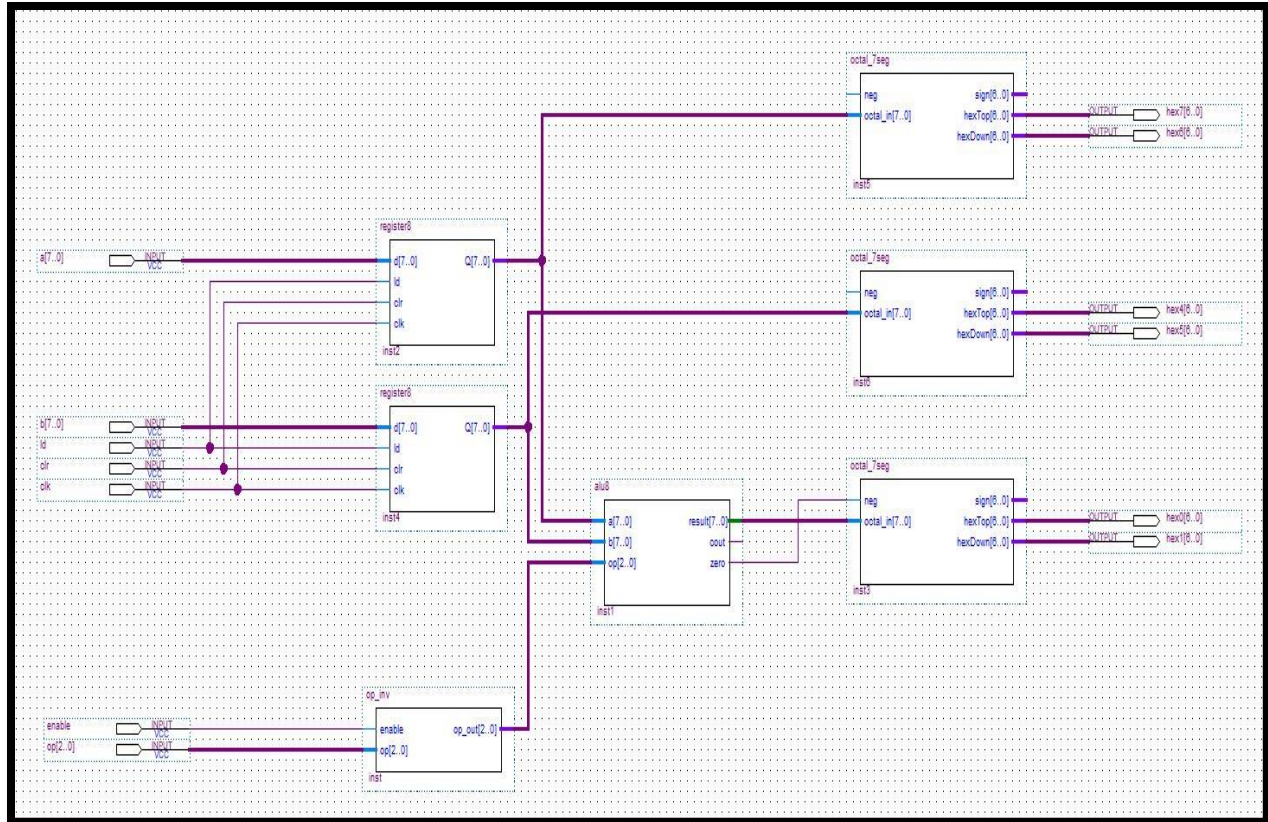


Figure 5: 8-bit ALU Schematic

Observations and Results

Figure 6, Figure 7, Figure 8, Figure 9, Figure 10, Figure 11, Figure 12, and Figure 13 are the waveform results of both functional and timing for the 8-bit ALU.

8-bit Register: Functional and Timing Waveforms

 


Figure 6: 8-bit register functional waveform

 


Figure 7: -bit register timing waveform

BCD to 7-segment converter: Functional and Timing Waveforms

 


Figure 8:: BCD to 7-segment display functional waveform

 


Figure 9: BCD to 7-segment display timing waveform

Operational Inverter: Functional and Timing Waveforms

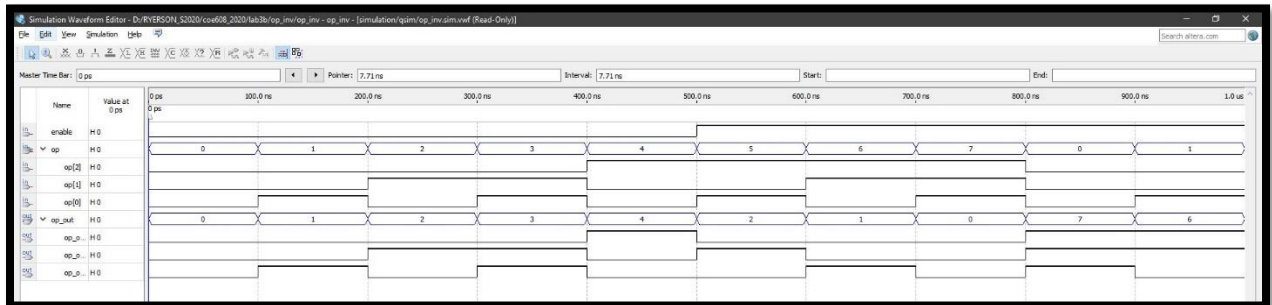


Figure 10: Op-inverter functional waveform

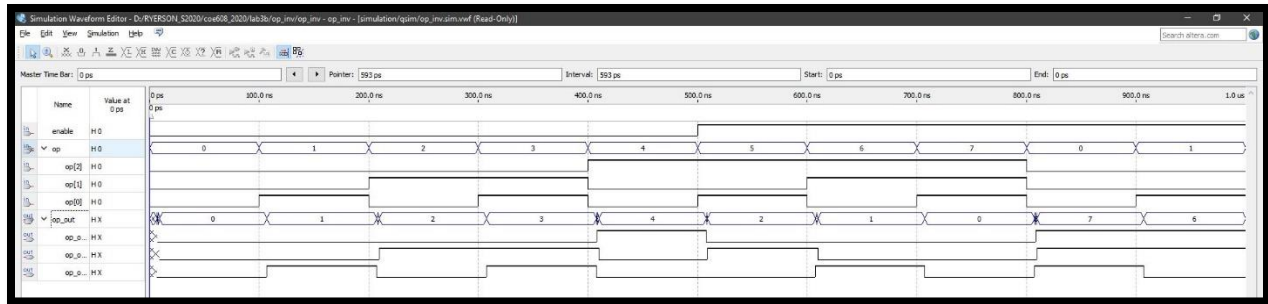


Figure 11: Op-inverter timing waveform

8-bit ALU: Functional and Timing Waveforms

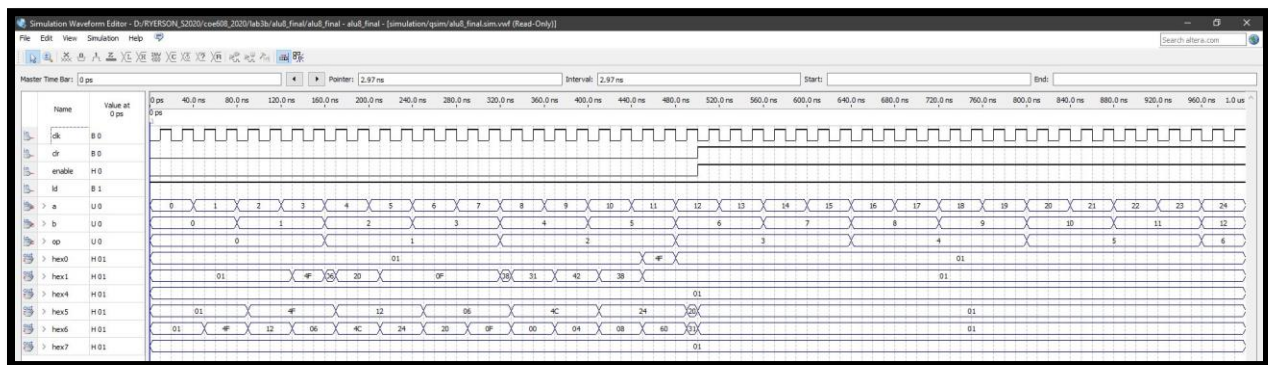


Figure 12: 8-bit ALU functional waveform

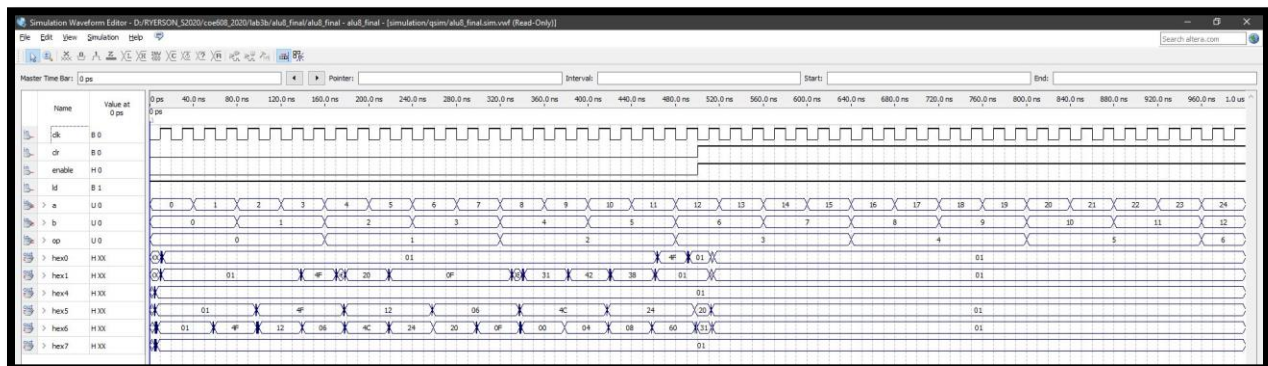


Figure 13: 8-bit ALU timing waveform


Appendices: VHDL Codes for the ALU, 7-segment displays, 8-bit register, and op inverter

The files are attached as PDF to make this document easier to read.

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  use ieee.std_logic_unsigned.all;
5
6
7  entity adder8 is
8      port(
9          cin, mode: in std_logic;
10         x, y : in std_logic_vector(31 downto 0);
11         s: out std_logic_vector(31 downto 0);
12         cout: out std_logic);
13 end adder8;
14
15 architecture description of adder8 is
16     signal c7, c6, c5, c4, c3, c2, c1, c0: std_logic;
17     component adder
18         port(
19             x, y, mode, cin: in std_logic;
20             cout, s : out std_logic);
21     end component adder;
22     begin
23         st0: adder port map (x(0), y(0), mode, mode, c1, s(0));
24         st1: adder port map (x(1), y(1), mode, c1, c2, s(1));
25         st2: adder port map (x(2), y(2), mode, c2, c3, s(2));
26         st3: adder port map (x(3), y(3), mode, c3, c4, s(3));
27         st4: adder port map (x(4), y(4), mode, c4, c5, s(4));
28         st5: adder port map (x(5), y(5), mode, c5, c6, s(5));
29         st6: adder port map (x(6), y(6), mode, c6, c7, s(6));
30         st7: adder port map (x(7), y(7), mode, c7, cout, s(7));
31     end description;
32
33
34
35
36
37
38
39
40
41
42
43
44
```




 
Master Time Bar: 0 ps Pointer: Interval: Start: End:





 Master Time Bar: 0 ps Pointer: 80.06 ns Interval: 80.06 ns Start: 0 ps End: 0 ps





```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  use ieee.std_logic_unsigned.all;
5  use ieee.numeric_std.all;
6
7  entity alu8 is
8      port(
9          a, b: in std_logic_vector(7 downto 0);
10         op: in std_logic_vector(2 downto 0);
11         result: inout std_logic_vector(7 downto 0);
12         cout, zero: out std_logic);
13 end alu8;
14
15 architecture description of alu8 is
16     component adder8 is
17         port(
18             cin, mode: in std_logic;
19             x, y: in std_logic_vector(7 downto 0);
20             s : out std_logic_vector(7 downto 0);
21             cout: out std_logic);
22     end component adder8;
23     signal addd: std_logic_vector(7 downto 0);
24     signal coutplus: std_logic;
25     signal shift: std_logic_vector(7 downto 0);
26     begin
27         muxadd: adder8 port map (op(2), op(2), a, b, addd, coutplus);
28         process (op)
29             begin
30                 if op = "000" then
31                     result <= a and b;
32                 elsif op = "001" then
33                     result <= a or b;
34                 elsif op = "010" then
35                     result <= addd;
36                     cout <= coutplus;
37                 elsif op = "110" then
38                     result <= addd;
39                     cout <= coutplus;
40                 elsif op = "100" then
41                     shift(0) <= a(7);
42                     shift(7 downto 1) <= a(6 downto 0);
43                     result <= shift;
44                 elsif op = "101" then
45                     shift(7) <= a(0);
46                     shift(6 downto 0) <= a(7 downto 1);
47                     result <= shift;
48                 else
49                     result <= (others => '0');
50                 end if;
51
52                 if result = "00000000" then
53                     zero <= '1';
54                 else
55                     zero <= '0';
56                 end if;
57             end process;
58         end description;
59
60 end description;
```

```
1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3
4  LIBRARY work;
5
6  ENTITY alu8_final IS
7      PORT
8      (
9          enable : IN STD_LOGIC;
10         ld : IN STD_LOGIC;
11         clr : IN STD_LOGIC;
12         clk : IN STD_LOGIC;
13         a : IN STD_LOGIC_VECTOR (7 DOWNTO 0);
14         b : IN STD_LOGIC_VECTOR (7 DOWNTO 0);
15         op : IN STD_LOGIC_VECTOR (2 DOWNTO 0);
16         hex0 : OUT STD_LOGIC_VECTOR (6 DOWNTO 0);
17         hex1 : OUT STD_LOGIC_VECTOR (6 DOWNTO 0);
18         hex4 : OUT STD_LOGIC_VECTOR (6 DOWNTO 0);
19         hex5 : OUT STD_LOGIC_VECTOR (6 DOWNTO 0);
20         hex6 : OUT STD_LOGIC_VECTOR (6 DOWNTO 0);
21         hex7 : OUT STD_LOGIC_VECTOR (6 DOWNTO 0)
22     );
23 END alu8_final;
24
25 ARCHITECTURE bdf_type OF alu8_final IS
26
27 COMPONENT op_inv
28     PORT(enable : IN STD_LOGIC;
29         op : IN STD_LOGIC_VECTOR (2 DOWNTO 0);
30         op_out : OUT STD_LOGIC_VECTOR (2 DOWNTO 0)
31     );
32 END COMPONENT;
33
34 COMPONENT alu8
35     PORT(a : IN STD_LOGIC_VECTOR (7 DOWNTO 0);
36         b : IN STD_LOGIC_VECTOR (7 DOWNTO 0);
37         op : IN STD_LOGIC_VECTOR (2 DOWNTO 0);
38         result : INOUT STD_LOGIC_VECTOR (7 DOWNTO 0);
39         cout : OUT STD_LOGIC;
40         zero : OUT STD_LOGIC
41     );
42 END COMPONENT;
43
44 COMPONENT register8
45     PORT(ld : IN STD_LOGIC;
46         clr : IN STD_LOGIC;
47         clk : IN STD_LOGIC;
48         d : IN STD_LOGIC_VECTOR (7 DOWNTO 0);
49         Q : OUT STD_LOGIC_VECTOR (7 DOWNTO 0)
50     );
51 END COMPONENT;
52
53 COMPONENT octal_7seg
54     PORT(neg : IN STD_LOGIC;
55         octal_in : IN STD_LOGIC_VECTOR (7 DOWNTO 0);
56         hexDown : OUT STD_LOGIC_VECTOR (6 DOWNTO 0);
57         hexTop : OUT STD_LOGIC_VECTOR (6 DOWNTO 0);
58         sign : OUT STD_LOGIC_VECTOR (6 DOWNTO 0)
59     );
60 END COMPONENT;
61
62 SIGNAL SYNTHESIZED_WIRE_7 : STD_LOGIC_VECTOR (7 DOWNTO 0);
```

```
63  SIGNAL    SYNTHESIZED_WIRE_8 :  STD_LOGIC_VECTOR (7 DOWNTO 0);
64  SIGNAL    op_inv1 :  STD_LOGIC_VECTOR (2 DOWNTO 0);
65  SIGNAL    zero1 :  STD_LOGIC;
66  SIGNAL    SYNTHESIZED_WIRE_4 :  STD_LOGIC_VECTOR (7 DOWNTO 0);
67
68
69  BEGIN
70
71
72
73  b2v_inst : op_inv
74  PORT MAP(enable => enable,
75           op => op,
76           op_out => op_inv1);
77
78
79  b2v_inst1 : alu8
80  PORT MAP(a => A_2_ALU,
81          b => B_2_ALU,
82          op => op_inv1,
83          result => result1,
84          zero => zero1);
85
86
87  b2v_inst2 : register8
88  PORT MAP(ld => ld,
89          clr => clr,
90          clk => clk,
91          d => a,
92          Q => A_2_ALU);
93
94
95  b2v_inst3 : octal_7seg
96  PORT MAP(neg => zero1,
97          octal_in => result1,
98          hexDown => hex1,
99          hexTop => hex0);
100
101
102  b2v_inst4 : register8
103  PORT MAP(ld => ld,
104          clr => clr,
105          clk => clk,
106          d => b,
107          Q => B_2_ALU);
108
109
110  b2v_inst5 : octal_7seg
111  PORT MAP(octal_in => A_2_ALU,
112          hexDown => hex6,
113          hexTop => hex7);
114
115
116  b2v_inst6 : octal_7seg
117  PORT MAP(octal_in => B_2_ALU,
118          hexDown => hex5,
119          hexTop => hex4);
120
121
122  END bdf_type;
```



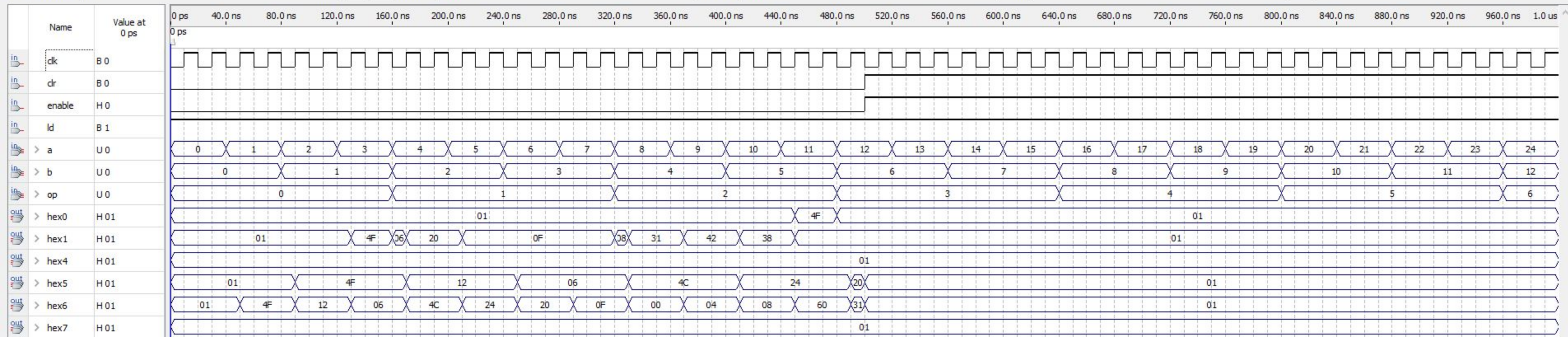

Master Time Bar: 0 ps


Pointer: 2.97 ns

Interval: 2.97 ns

Start:

End:



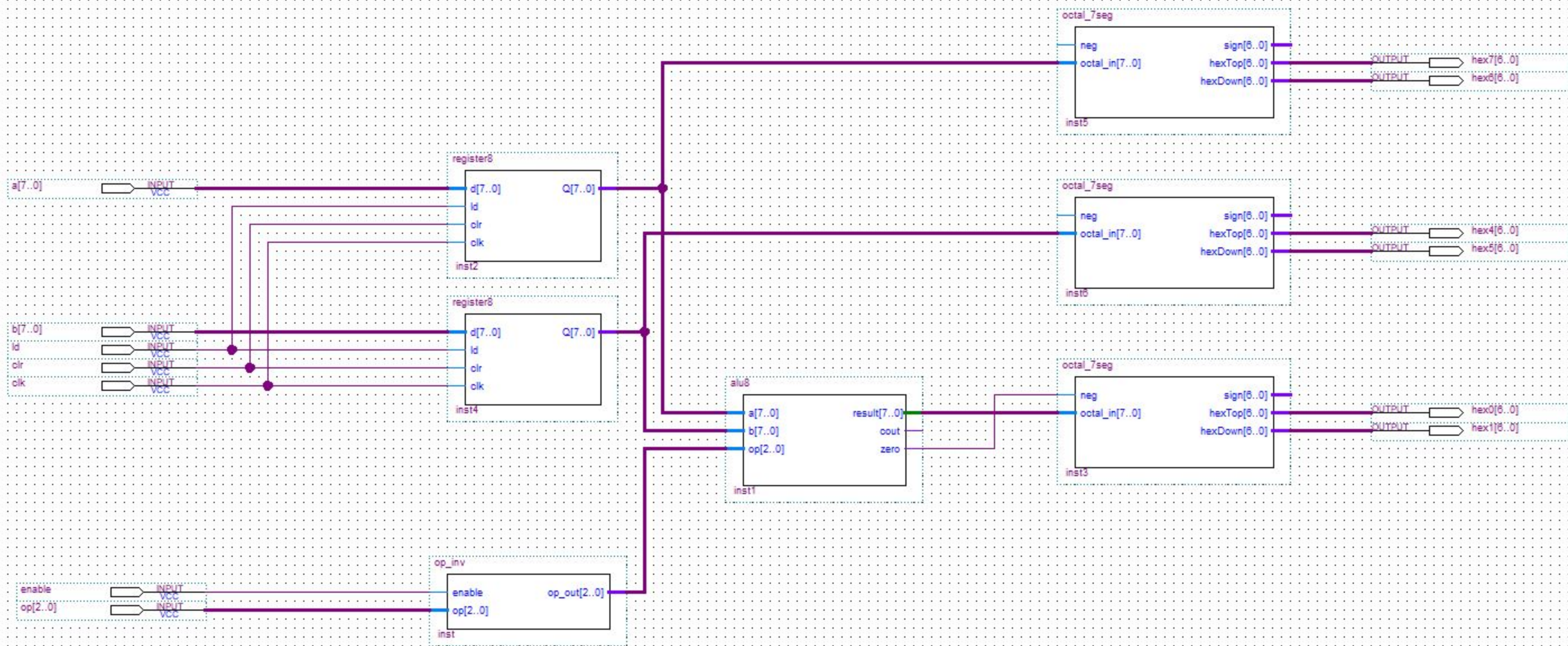



Master Time Bar: 0 ps




Pointer:

Interval:


Start:


End:

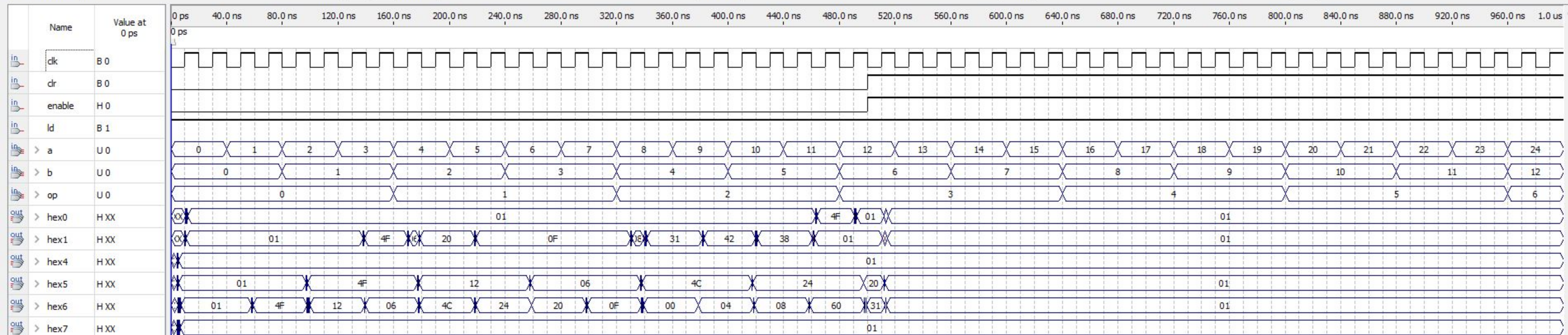




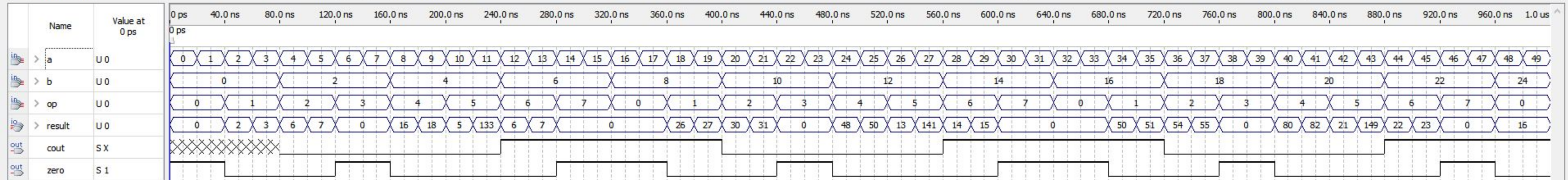
Master Time Bar: 0 ps ◀ ▶ Pointer: 29.65 ns Interval: 29.65 ns Start: End:



 

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  use ieee.std_logic_unsigned.all;
5  use ieee.numeric_std.all;
6  use ieee.numeric_bit.all;
7
8  entity bcd7seg is
9      port(
10         bcd_in: in std_logic_vector(3 downto 0);
11         sevenseg: out std_logic_vector(6 downto 0));
12 end bcd7seg;
13
14 architecture behavior of bcd7seg is
15     begin
16         process(bcd_in)
17             begin
18                 case bcd_in is
19                     when "0000" => sevenseg <= "0000001"; --0
20                     when "0001" => sevenseg <= "1001111"; --1
21                     when "0010" => sevenseg <= "0010010"; --2
22                     when "0011" => sevenseg <= "0000110"; --3
23                     when "0100" => sevenseg <= "1001100"; --4
24                     when "0101" => sevenseg <= "0100100"; --5
25                     when "0110" => sevenseg <= "0100000"; --6
26                     when "0111" => sevenseg <= "0001111"; --7
27                     when "1000" => sevenseg <= "0000000"; --8
28                     when "1001" => sevenseg <= "0000100"; --9
29                     when "1010" => sevenseg <= "0001000"; --A
30                     when "1011" => sevenseg <= "1100000"; --b
31                     when "1100" => sevenseg <= "0110001"; --C
32                     when "1101" => sevenseg <= "1000010"; --d
33                     when "1110" => sevenseg <= "0110000"; --E
34                     when "1111" => sevenseg <= "0111000"; --F
35                 end case;
36             end process;
37         end behavior;
38
39
```

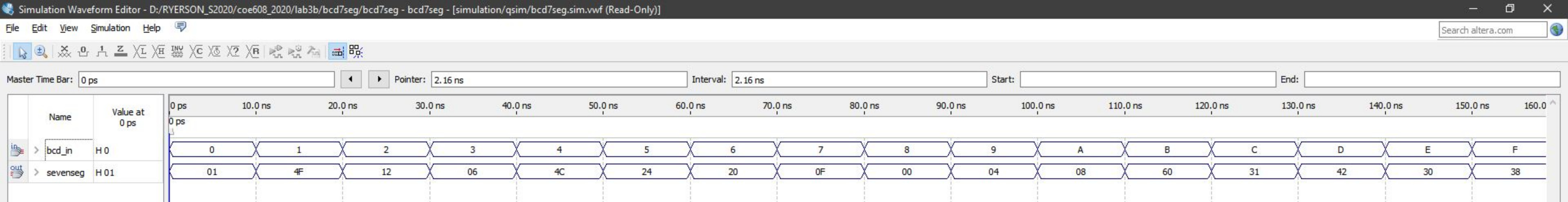

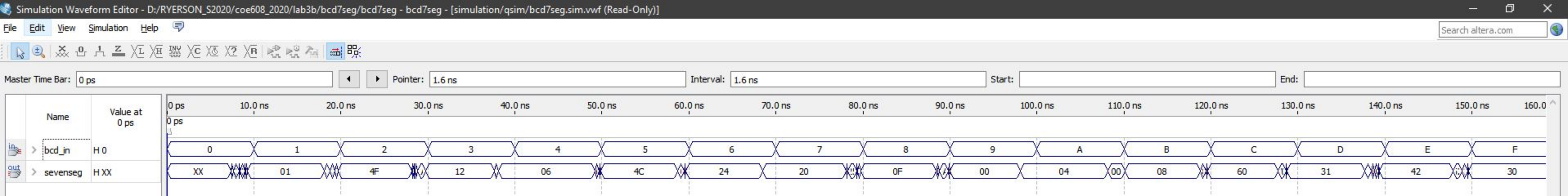

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  use ieee.std_logic_unsigned.all;
5  use ieee.numeric_bit.all;
6  use ieee.numeric_std.all;
7  use ieee.std_logic_misc.all;
8
9  entity octal_7seg is
10     port(
11         neg : in std_logic;
12         octal_in : in std_logic_vector(7 downto 0);
13         sign, hexTop, hexDown : out std_logic_vector(6 downto 0));
14 end octal_7seg;
15
16 architecture behavior of octal_7seg is
17     signal bcdTop, bcdDown : std_logic_vector(3 downto 0);
18     begin
19         process(octal_in)
20             begin
21                 bcdTop <= octal_in(7 downto 4);
22                 bcdDown <= octal_in(3 downto 0);
23                 case bcdTop is
24                     when "0000" => hexTop <= "0000001"; --0
25                     when "0001" => hexTop <= "1001111"; --1
26                     when "0010" => hexTop <= "0010010"; --2
27                     when "0011" => hexTop <= "0000110"; --3
28                     when "0100" => hexTop <= "1001100"; --4
29                     when "0101" => hexTop <= "0100100"; --5
30                     when "0110" => hexTop <= "0100000"; --6
31                     when "0111" => hexTop <= "0001111"; --7
32                     when "1000" => hexTop <= "0000000"; --8
33                     when "1001" => hexTop <= "0000100"; --9
34                     when "1010" => hexTop <= "0001000"; --A
35                     when "1011" => hexTop <= "1100000"; --b
36                     when "1100" => hexTop <= "0110001"; --C
37                     when "1101" => hexTop <= "1000010"; --d
38                     when "1110" => hexTop <= "0110000"; --E
39                     when "1111" => hexTop <= "0111000"; --F
40                     when others => hexTop <= (others => '0');
41                 end case;
42                 case bcdDown is
43                     when "0000" => hexDown <= "0000001"; --0
44                     when "0001" => hexDown <= "1001111"; --1
45                     when "0010" => hexDown <= "0010010"; --2
46                     when "0011" => hexDown <= "0000110"; --3
47                     when "0100" => hexDown <= "1001100"; --4
48                     when "0101" => hexDown <= "0100100"; --5
49                     when "0110" => hexDown <= "0100000"; --6
50                     when "0111" => hexDown <= "0001111"; --7
51                     when "1000" => hexDown <= "0000000"; --8
52                     when "1001" => hexDown <= "0000100"; --9
53                     when "1010" => hexDown <= "0001000"; --A
54                     when "1011" => hexDown <= "1100000"; --b
55                     when "1100" => hexDown <= "0110001"; --C
56                     when "1101" => hexDown <= "1000010"; --d
57                     when "1110" => hexDown <= "0110000"; --E
58                     when "1111" => hexDown <= "0111000"; --F
59                     when others => hexDown <= (others => '0');
60                 end case;
61                 if neg = '0' then
62                     sign <= "1111110";
```

```
63         elsif neg = '1' then
64             sign <= "1111111";
65         end if;
66     end process;
67 end behavior;
68
```



Master Time Bar: 0 ps




Pointer:

Interval:

Start:

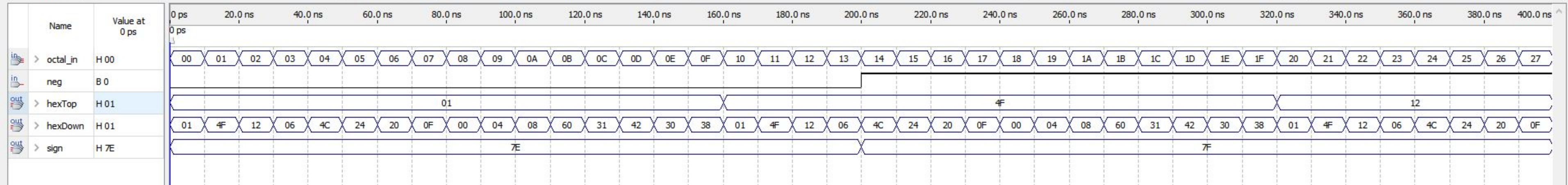


 

End:





0 ps




		Name	Value at 0 ps	0 ps	20.0 ns	40.0 ns	60.0 ns	80.0 ns	100.0 ns	120.0 ns	140.0 ns	160.0 ns	180.0 ns	200.0 ns	220.0 ns	240.0 ns	260.0 ns	280.0 ns	300.0 ns	320.0 ns	340.0 ns	360.0 ns	380.0 ns	400.0 ns							
				0 ps																											
	>	octal_in	H 00	<div>000102030405060708090A0B0C0D0E0F101112131415161718191A1B1C1D1E1F2021222324252627</div>																											
		neg	B 0	<div></div>																											
	>	hexTop	H XX	<div>XX014F12</div>																											
	>	hexDown	H XX	<div>XX014F12064C24200F0004086031423038014F12064C24200F0004086031423038014F12064C2420</div>																											
	>	sign	H 7X	<div>7X7E7F</div>																											

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  use ieee.std_logic_unsigned.all;
5
6  entity octal_bcd_conv is
7      port(
8          input_8 : in std_logic_vector(7 downto 0);
9          out_top4: out std_logic_vector(3 downto 0);
10         out_bot4 : out std_logic_vector(3 downto 0));
11 end octal_bcd_conv;
12
13 architecture behavior of octal_bcd_conv is
14     begin
15         process(input_8)
16             begin
17                 out_top4 <= input_8(7 downto 4);
18                 out_bot4 <= input_8(3 downto 0);
19             end process;
20 end behavior;
21
22
```




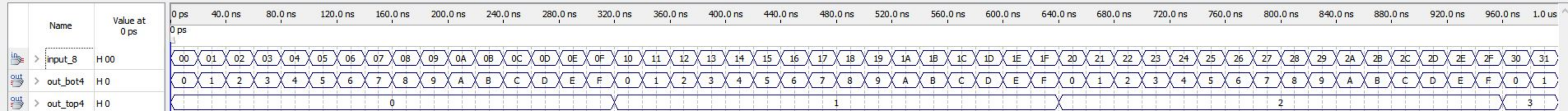
Master Time Bar: 0 ps Pointer: 8.9 ns Interval: 8.9 ns Start: End:





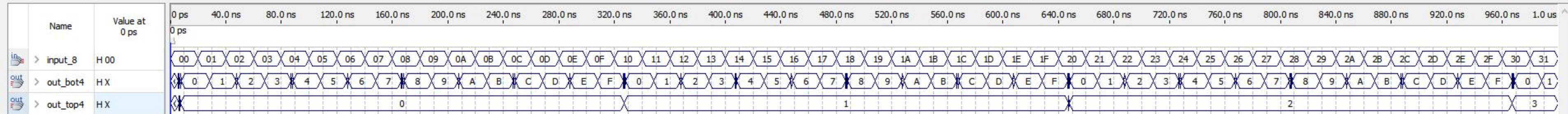
Master Time Bar: 0 ps Pointer: Interval: Start: End:



```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  use ieee.std_logic_unsigned.all;
5
6  entity op_inv is
7      port(
8          enable: in std_logic;
9          op: in std_logic_vector(2 downto 0);
10         op_out : out std_logic_vector (2 downto 0));
11 end op_inv;
12
13 architecture behavior of op_inv is
14     begin
15         process(enable, op)
16             begin
17                 if enable = '0' then
18                     op_out <= op;
19                 elsif enable = '1' then
20                     op_out <= not op;
21                 else
22                     op_out <= "---";
23                 end if;
24             end process;
25 end behavior;
26
27
28
```



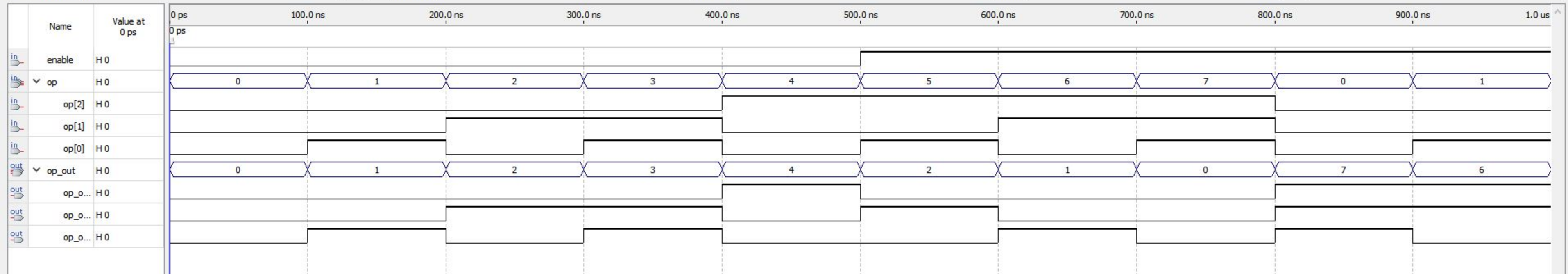Master Time Bar: 0 ps Pointer: 7.71 ns Interval: 7.71 ns Start: End:






Master Time Bar: 0 ps

Pointer: 593 ps

Interval: 593 ps

Start: 0 ps

End: 0 ps

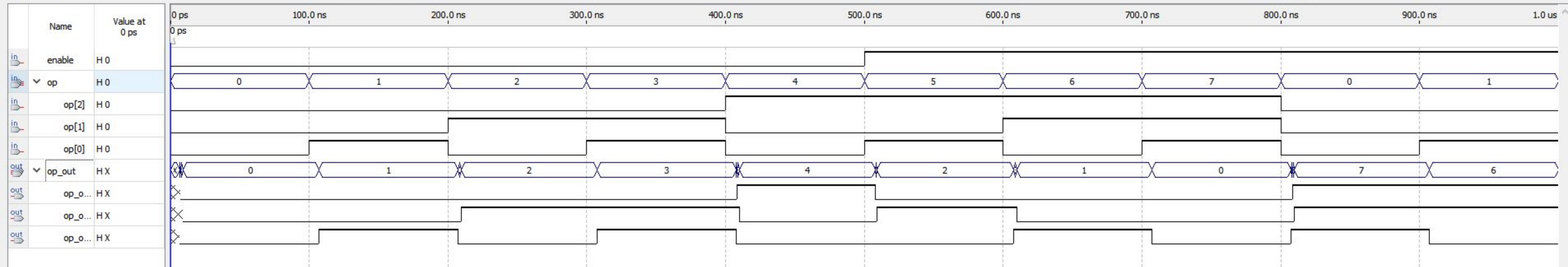

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  use ieee.std_logic_unsigned.all;
5  entity register8 is
6      port (
7          d: in std_logic_vector(7 downto 0);
8          ld,clr,clk: in std_logic;
9          Q: out std_logic_vector(7 downto 0));
10 end register8;
11
12 architecture description of register8 is
13     begin
14         process (ld,clr,clk)
15             begin
16                 if ld = '0' or clr = '1' then
17                     Q <= (others => '0');
18                 elsif rising_edge(clk) then
19                     Q <= d;
20                 end if;
21             end process;
22 end description;
23
24
```



 

Master Time Bar: 0 ps

Pointer: 8.9 ns

Interval: 8.9 ns

Start:

End:





Master Time Bar: 0 ps Pointer: Interval: Start: End:

