

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  use ieee.std_logic_unsigned.all;
5
6
7  entity adder8 is
8      port(
9          cin, mode: in std_logic;
10         x, y : in std_logic_vector(31 downto 0);
11         s: out std_logic_vector(31 downto 0);
12         cout: out std_logic);
13 end adder8;
14
15 architecture description of adder8 is
16     signal c7, c6, c5, c4, c3, c2, c1, c0: std_logic;
17     component adder
18         port(
19             x, y, mode, cin: in std_logic;
20             cout, s : out std_logic);
21     end component adder;
22     begin
23         st0: adder port map (x(0), y(0), mode, mode, c1, s(0));
24         st1: adder port map (x(1), y(1), mode, c1, c2, s(1));
25         st2: adder port map (x(2), y(2), mode, c2, c3, s(2));
26         st3: adder port map (x(3), y(3), mode, c3, c4, s(3));
27         st4: adder port map (x(4), y(4), mode, c4, c5, s(4));
28         st5: adder port map (x(5), y(5), mode, c5, c6, s(5));
29         st6: adder port map (x(6), y(6), mode, c6, c7, s(6));
30         st7: adder port map (x(7), y(7), mode, c7, cout, s(7));
31     end description;
32
33
34
35
36
37
38
39
40
41
42
43
44
```