

Name: Xinyu Hadrian Hu, and Duan Wei Zhang

Student Number: 500194233, and 500824903

Date: June 26, 2020

COE 608: Computer Architecture and Design

COE 608: Lab 3, Part 1 Report

Purpose

The purpose of this lab is to generate the components of a 32-bit ALU, with six different operations. The addition and subtraction units must be done in structural form of VHDL.

Design and Implementation

The goal of the 32-bit ALU is to perform the following operations:

32-bit ALU			
OP Name ▼	Neg/Tsel ▼	ALU-Select ▼	Operation Performed ▼
AND (logical)	0	00	Result \leq a AND b
OR (logical)	0	01	Result \leq a OR b
ADD	0	10	Result \leq a + b
SUB	1	10	Result \leq a - b
ROL	1	00	Result \leq a \ll 1
ROR	1	01	Result \leq a \gg 1

Figure 1: ALU Operations

The first step is to create the adder, since it is not possible to use behavioral model in this lab to create the adder circuit.

Full Adder Truth Table				
A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1
		Sum	A xor B xor C	
		Cout	(A and (B or C)) or (B and C)	

Figure 2: Full Adder Circuit with logical functions

Next, the operation of the two-to-one multiplexer is illustrated below:

2 to 1 Multiplexer					
A	B	X	A and not X	B and X	A and not X or (B and X)
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	1	1
1	0	0	1	0	1
1	0	1	0	0	0
1	1	0	0	0	0
1	1	1	0	1	1

Figure 3: Two-to-one multiplexer

Next, the binary-coded-decimal to seven-segment converter is shown below. It is assumed that the seven-segment display is cathode-active.

BCD to 7 segment display		
BCD Code ▼	7seg Code ▼	Symbol ▼
0 0 0 0	0 0 0 0 0 0 1	0
0 0 0 1	1 0 0 1 1 1 1	1
0 0 1 0	0 0 1 0 0 1 0	2
0 0 1 1	0 0 0 0 1 1 0	3
0 1 0 0	1 0 0 1 1 0 0	4
0 1 0 1	0 1 0 0 1 0 0	5
0 1 1 0	0 1 0 0 0 0 0	6
0 1 1 1	0 0 0 1 1 1 1	7
1 0 0 0	0 0 0 0 0 0 0	8
1 0 0 1	0 0 0 0 1 0 0	9
1 0 1 0	0 0 0 1 0 0 0	A
1 0 1 1	1 1 0 0 0 0 0	B
1 1 0 0	0 1 1 0 0 0 1	C
1 1 0 1	1 0 0 0 0 1 0	D
1 1 1 0	0 1 1 0 0 0 0	E
1 1 1 1	0 1 1 1 0 0 0	F

Figure 4: BCD to 7 segment display Truth Table

One-bit Adder: Functional and Timing Waveforms

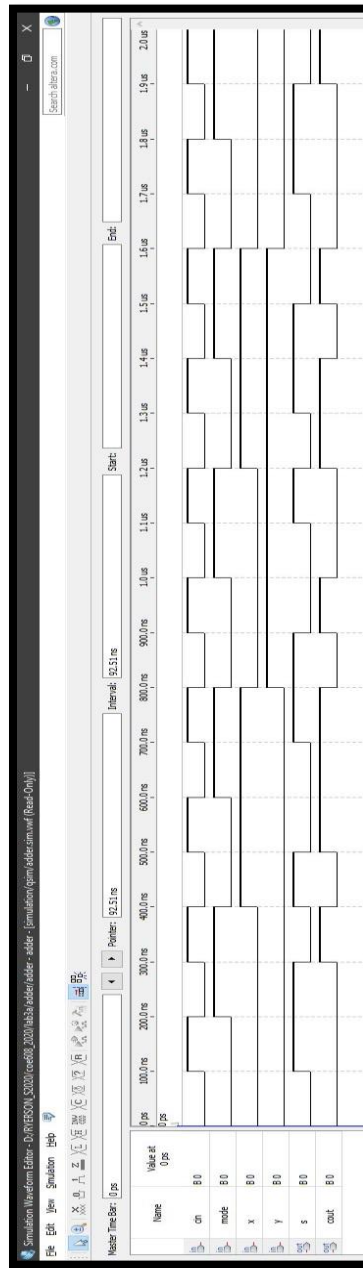


Figure 5: 1-bit Adder Functional Waveform

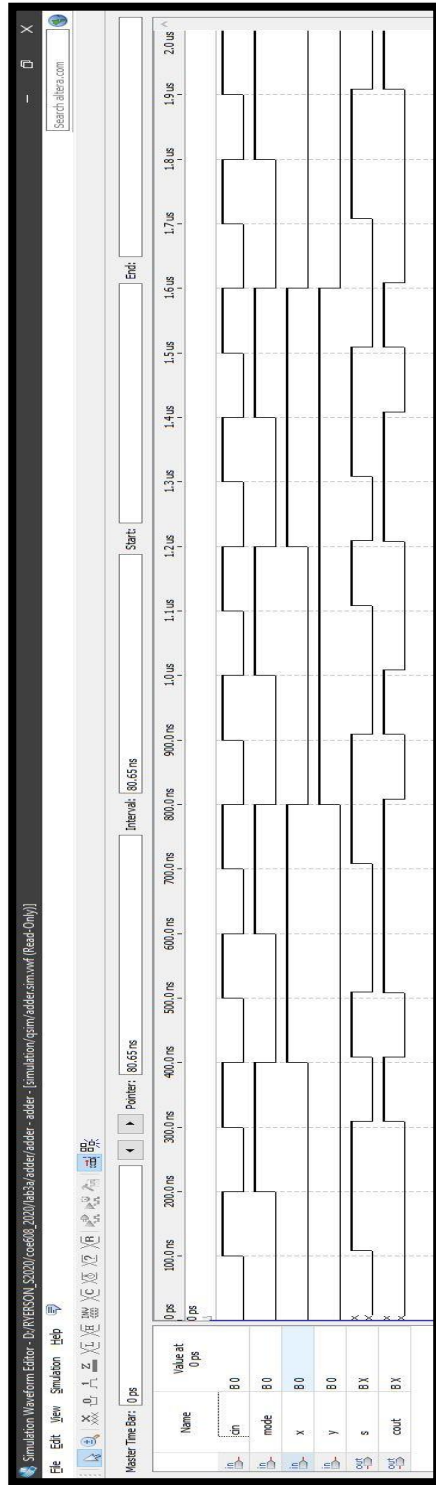


Figure 6: 1-bit Adder Timing Waveform

32-bit Adder: Functional and Timing Waveforms

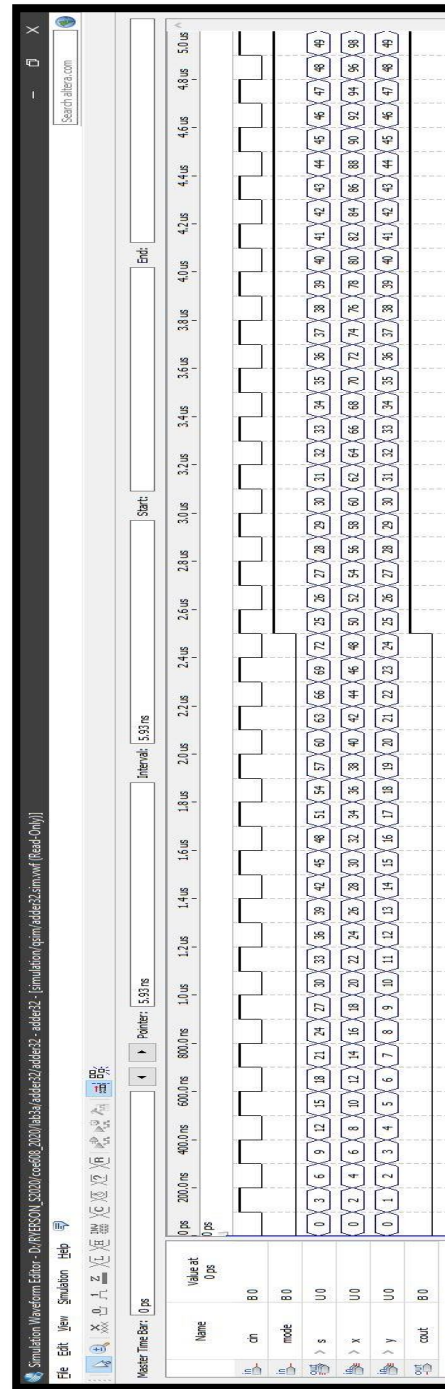


Figure 7: 32-bit Adder Functional Waveform

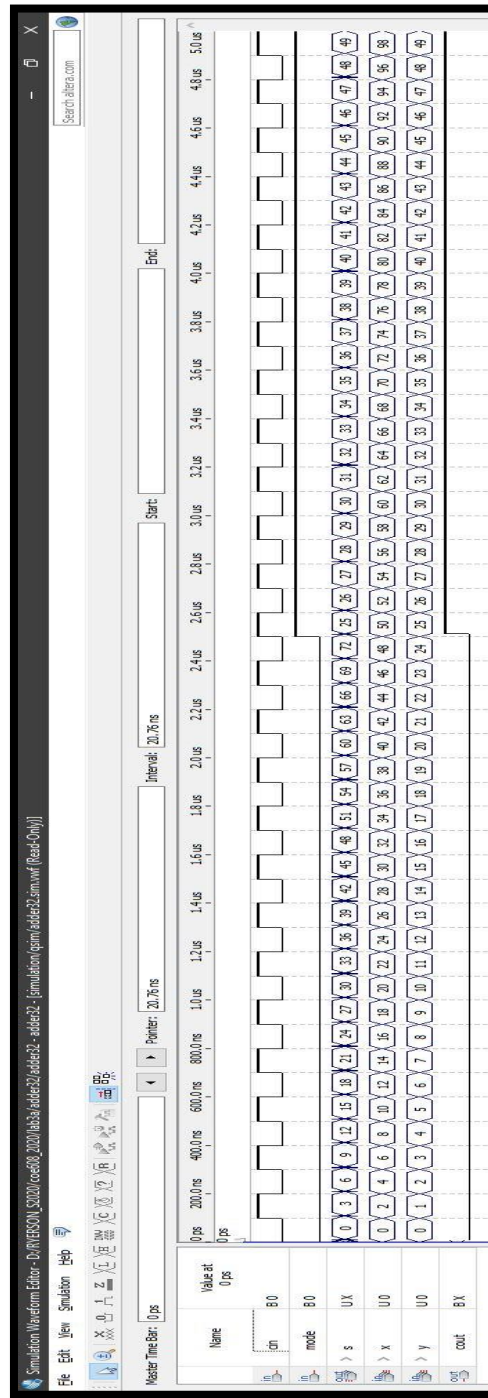


Figure 8: 32-bit Adder Timing Waveform

2 to 1 Multiplexer: Functional and Timing Waveforms

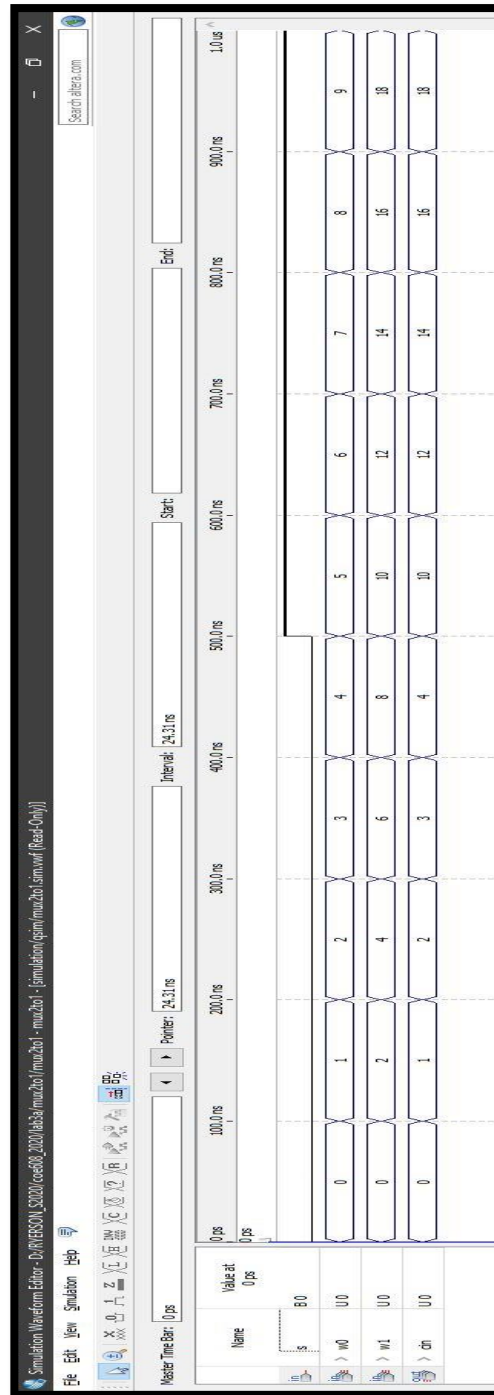


Figure 9: 2-to1 Multiplexer Functional Waveform

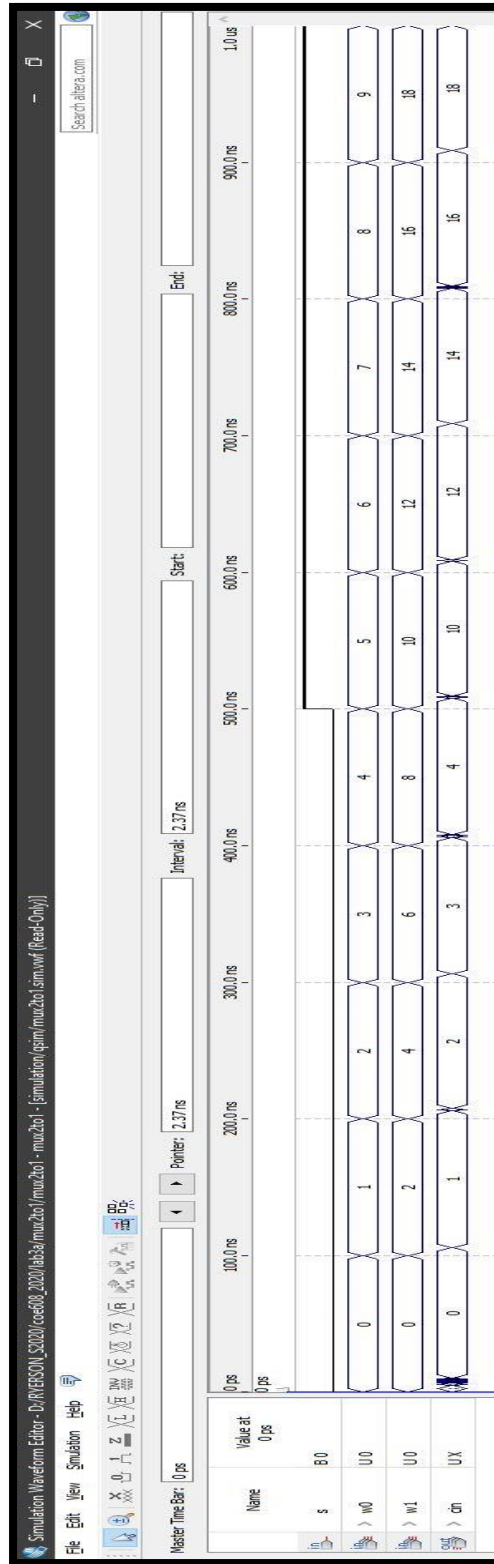


Figure 10: 2-to-1 Multiplexer Timing Waveform

32-bit ALU: Functional and Timing Waveforms


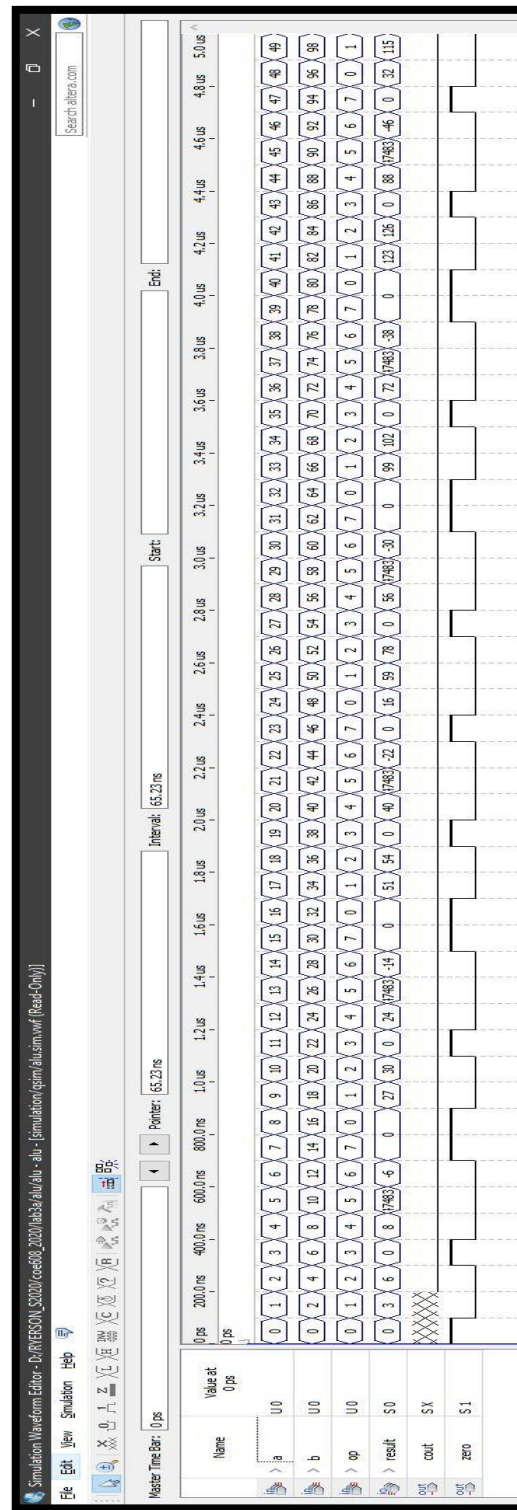


Figure 11: 32-bit ALU Functional Waveform

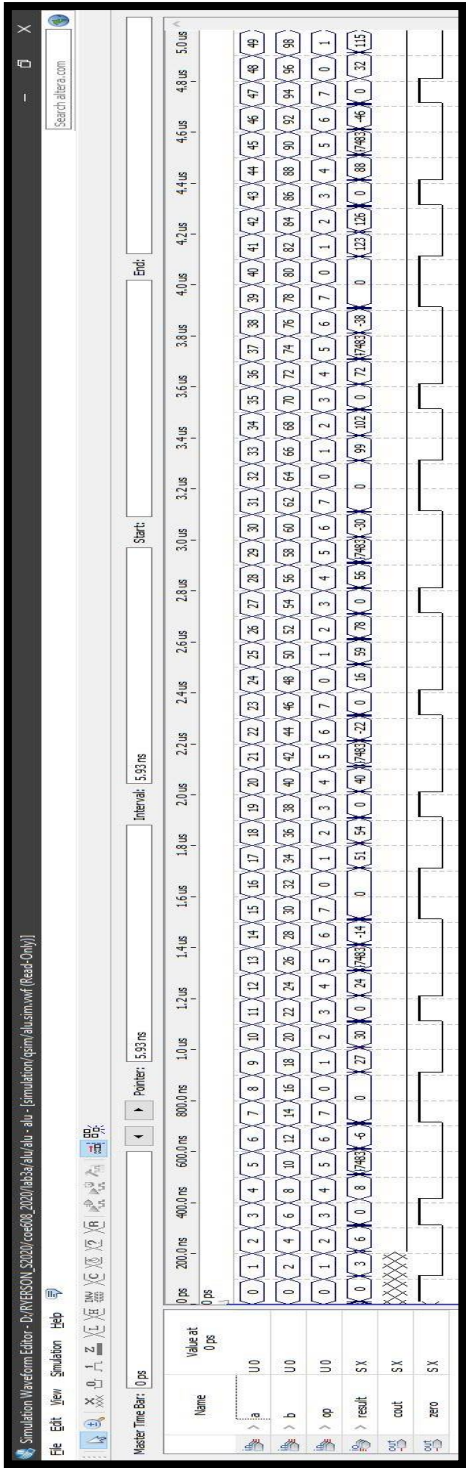

Discussions and Conclusions

All of the above devices work as expected. The worst-case delay of the 32-bit ALU is 1 ns, for most outputs. The longest delay occurs at the positive or negative signs of the output. The worst delay for the negative output symbol is 40 ns.


Appendices: VHDL Codes for the ALU and other Supporting Devices

The files are attached as PDF to make this document easier to read.

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  use ieee.std_logic_unsigned.all;
5
6  entity adder is
7      port (
8          x, y: in std_logic;
9          mode: in std_logic;
10         cin : in std_logic;
11         cout : out std_logic;
12         s : out std_logic);
13 end adder;
14
15 architecture behavior of adder is
16     signal temp : std_logic;
17     begin
18         process(mode)
19             begin
20                 if (mode = '1') then
21                     temp <= (y xor mode);
22                 else
23                     temp <= y;
24                 end if;
25                 s <= (x xor temp xor cin) or (x and temp and cin);
26                 cout <= (x and temp) or (x and cin) or (cin and temp);
27             end process;
28 end behavior;
29
30
31
```




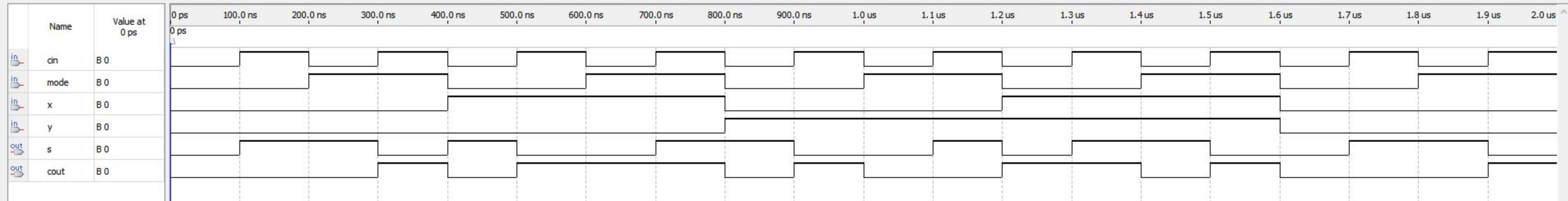Master Time Bar: 0 ps Pointer: 92.51 ns Interval: 92.51 ns Start: End:





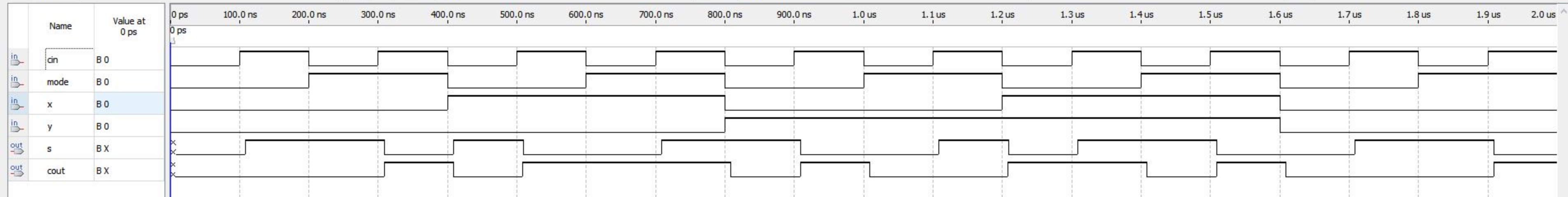Master Time Bar: 0 ps Pointer: 80.65 ns Interval: 80.65 ns Start: End:



```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  use ieee.std_logic_unsigned.all;
5
6  ENTITY adder32 IS
7      PORT(cin          :IN STD_LOGIC;
8           mode         :IN STD_LOGIC; -- 1 = sub , 0 = add
9           x            : in std_logic_vector(31 downto 0);
10          y            : in std_logic_vector(31 downto 0);
11          s            : out std_logic_vector(31 downto 0);
12          cout         :OUT STD_LOGIC
13      );
14  end adder32;
15
16  ARCHITECTURE description of adder32 IS
17      SIGNAL c31,c30,c29,c28,c27,c26,c25,c24,c23,c22,c21,c20,c19,c18,c17,c16,c15,c14,c13,c12,
18      c11,c10,c9,c8,c7,c6,c5,c4,c3,c2,c1,c0 : STD_LOGIC;
19      COMPONENT adder
20          port(
21              x : in std_logic;
22              y : in std_logic;
23              mode : in std_logic;
24              cin : in std_logic;
25              cout : out std_logic;
26              s : out std_logic
27          );
28      END COMPONENT;
29  BEGIN
30      --st0: adder port map (x(0), y(0), mode, cin, c1, s(0));
31      st0: adder port map (x(0), y(0), mode, mode, c1, s(0));
32      st1: adder port map (x(1), y(1), mode, c1, c2, s(1));
33      st2: adder port map (x(2), y(2), mode, c2, c3, s(2));
34      st3: adder port map (x(3), y(3), mode, c3, c4, s(3));
35      st4: adder port map (x(4), y(4), mode, c4, c5, s(4));
36      st5: adder port map (x(5), y(5), mode, c5, c6, s(5));
37      st6: adder port map (x(6), y(6), mode, c6, c7, s(6));
38      st7: adder port map (x(7), y(7), mode, c7, c8, s(7));
39      st8: adder port map (x(8), y(8), mode, c8, c9, s(8));
40      st9: adder port map (x(9), y(9), mode, c9, c10, s(9));
41      st10: adder port map (x(10), y(10), mode, c10, c11, s(10));
42      st11: adder port map (x(11), y(11), mode, c11, c12, s(11));
43      st12: adder port map (x(12), y(12), mode, c12, c13, s(12));
44      st13: adder port map (x(13), y(13), mode, c13, c14, s(13));
45      st14: adder port map (x(14), y(14), mode, c14, c15, s(14));
46      st15: adder port map (x(15), y(15), mode, c15, c16, s(15));
47      st16: adder port map (x(16), y(16), mode, c16, c17, s(16));
48      st17: adder port map (x(17), y(17), mode, c17, c18, s(17));
49      st18: adder port map (x(18), y(18), mode, c18, c19, s(18));
50      st19: adder port map (x(19), y(19), mode, c19, c20, s(19));
51      st20: adder port map (x(20), y(20), mode, c20, c21, s(20));
52      st21: adder port map (x(21), y(21), mode, c21, c22, s(21));
53      st22: adder port map (x(22), y(22), mode, c22, c23, s(22));
54      st23: adder port map (x(23), y(23), mode, c23, c24, s(23));
55      st24: adder port map (x(24), y(24), mode, c24, c25, s(24));
56      st25: adder port map (x(25), y(25), mode, c25, c26, s(25));
57      st26: adder port map (x(26), y(26), mode, c26, c27, s(26));
58      st27: adder port map (x(27), y(27), mode, c27, c28, s(27));
59      st28: adder port map (x(28), y(28), mode, c28, c29, s(28));
60      st29: adder port map (x(29), y(29), mode, c29, c30, s(29));
61      st30: adder port map (x(30), y(30), mode, c30, c31, s(30));
62      st31: adder port map (x(31), y(31), mode, c31, cout, s(31));
```



```
62     end description;  
63
```




Master Time Bar: 0 ps

Pointer: 5.93 ns

Interval: 5.93 ns


Start:

End:

 



 
Master Time Bar: 0 ps Pointer: 20.76 ns Interval: 20.76 ns Start: End:



```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  use ieee.std_logic_unsigned.all;
5  use ieee.numeric_std.all;
6
7  entity alu is
8      port(
9          a, b: in std_logic_vector(31 downto 0);
10         op: in std_logic_vector(2 downto 0);
11         result: inout std_logic_vector(31 downto 0);
12         cout, zero: out std_logic);
13 end alu;
14
15 architecture description of alu is
16     component adder32 is
17         port(
18             cin, mode: in std_logic;
19             x, y: in std_logic_vector(31 downto 0);
20             s : out std_logic_vector(31 downto 0);
21             cout: out std_logic);
22     end component adder32;
23     signal addd: std_logic_vector(31 downto 0);
24     signal coutplus: std_logic;
25     signal shift: std_logic_vector(31 downto 0);
26     begin
27         muxadd: adder32 port map (op(2), op(2), a, b, addd, coutplus);
28         process (op)
29             begin
30                 if op = "000" then
31                     result <= a and b;
32                 elsif op = "001" then
33                     result <= a or b;
34                 elsif op = "010" then
35                     result <= addd;
36                     cout <= coutplus;
37                 elsif op = "110" then
38                     result <= addd;
39                     cout <= coutplus;
40                 elsif op = "100" then
41                     shift(0) <= a(31);
42                     shift(31 downto 1) <= a(30 downto 0);
43                     result <= shift;
44                 elsif op = "101" then
45                     shift(31) <= a(0);
46                     shift(30 downto 0) <= a(31 downto 1);
47                     result <= shift;
48                 else
49                     result <= (others => '0');
50                 end if;
51
52                 if result = "000000000000000000000000000000" then
53                     zero <= '1';
54                 else
55                     zero <= '0';
56                 end if;
57             end process;
58         end description;
```



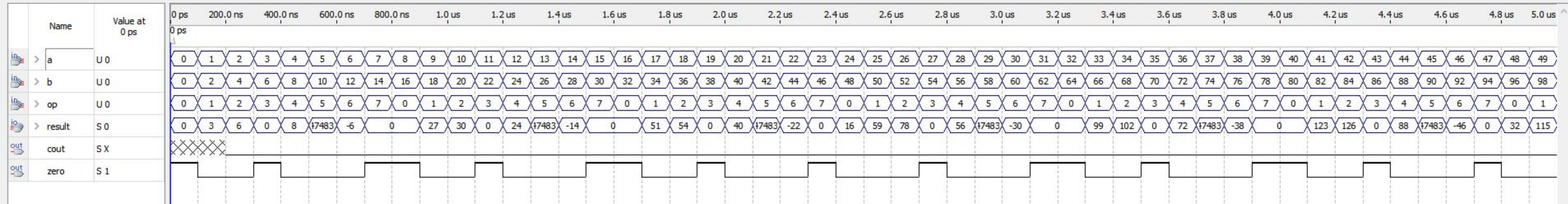Master Time Bar: 0 ps Pointer: 65.23 ns Interval: 65.23 ns Start: End:






Master Time Bar: 0 ps

Pointer: 5.93 ns

Interval: 5.93 ns

Start:

End:

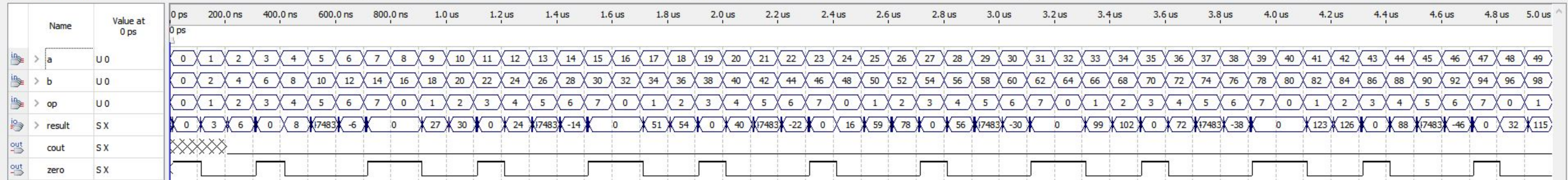

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  use ieee.std_logic_unsigned.all;
5  entity mux2tool is
6  port(
7      st : in std_logic;
8      w0,w1 : in std_logic;
9      cin : out std_logic
10     );
11     end mux2tool;
12
13 architecture description of mux2tool is begin
14     --if (st = '0') then -- st if start
15         --cin <= '0';
16     --elsif(st = '1')then
17         --cin <= '1';
18     --end if; --st if end
19 end description;
20
```




Master Time Bar: 0 ps

Pointer: 24.31 ns

Interval: 24.31 ns


Start:

End:

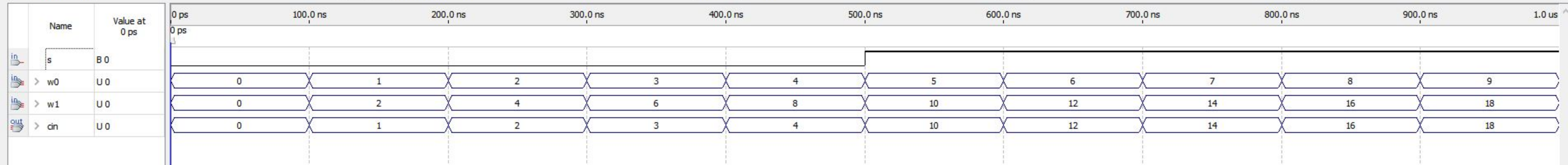



 Master Time Bar: 0 ps Pointer: 2.37 ns Interval: 2.37 ns Start: End:



```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_arith.all;
4  use ieee.std_logic_unsigned.all;
5
6  entity two_bit_asu is
7      port (
8          a, b: in std_logic_vector(1 downto 0);
9          add_sub: in std_logic;
10         result: out std_logic_vector(1 downto 0));
11 end two_bit_asu;
12
13 architecture behavior of two_bit_asu is
14     begin
15         process(a,b,add_sub)
16         begin
17             if add_sub = '0' then --adding
18                 result <= a or b;
19             elsif add_sub = '1' then --subtracting
20                 result <= (a or (not b))+ 1;
21             end if;
22         end process;
23     end behavior;
```



		0 ps40.0 ns80.0 ns120.0 ns160.0 ns200.0 ns240.0 ns280.0 ns320.0 ns360.0 ns400.0 ns440.0 ns480.0 ns520.0 ns560.0 ns600.0 ns640.0 ns680.0 ns720.0 ns760.0 ns800.0 ns840.0 ns880.0 ns920.0 ns960.0 ns1.0 us																													
		Name	Value at 0 ps	0 ps																											
in		add_sub	B 0																												
in	>	a	U 0																												
in	>	b	U 0																												
out	>	result	S 0																												



Master Time Bar: 0 ps

Pointer: 13.05 ns

Interval: 13.05 ns

Start: 0 ps

End: 0 ps

